

$$(723_{10})_2 = (?)_2$$

$$\begin{array}{r} 2 | \overline{723} \\ \underline{3} \quad \quad \quad 2 | 361 - 1 \\ \underline{1} \quad \quad \quad 2 | 180 - 1 \\ \underline{0} \quad \quad \quad 2 | 90 - 0 \\ \underline{0} \quad \quad \quad 2 | 45 - 0 \\ \underline{1} \quad \quad \quad 2 | 44 - 1 \\ \underline{1} \quad \quad \quad 2 | 22 - 0 \\ \underline{0} \quad \quad \quad 2 | 11 - 0 \\ \underline{1} \quad \quad \quad 2 | 10 - 1 \\ \underline{1} \quad \quad \quad 2 | 5 - 0 \\ \underline{1} \quad \quad \quad 2 | 3 - 1 \\ \underline{1} \quad \quad \quad 2 | 1 - 0 \\ \underline{1} \quad \quad \quad 2 | 0 - 1 \end{array}$$

$0 \cdot 8 \times 2 = 0 \cdot 6$
 $0 \cdot 6 \times 2 = 1 \cdot 2$
 $0 \cdot 2 \times 2 = 0 \cdot 4$
 $0 \cdot 4 \times 2 = 0 \cdot 8$
 $\underline{\underline{1100}}$
 $\underline{\underline{0000}}$

$$(101100000011.1100)_2$$

~~$$\begin{array}{r} 8 | \overline{723} \\ \underline{5} \quad \quad \quad 8 | 90 - 3 \\ \underline{3} \quad \quad \quad 8 | 11 - 2 \\ \underline{2} \quad \quad \quad 0 | 1 - 3 \\ \underline{3} \quad \quad \quad 0 | 0 - 1 \end{array}$$

$0 \cdot 8 \times 8 = 6 \cdot 4$
 $0 \cdot 4 \times 8 = 3 \cdot 2$
 $0 \cdot 2 \times 8 = 1 \cdot 6$
 $0 \cdot 6 \times 8 = 0 \cdot 8$~~

~~$$723_{10} = (1323.6314)_8$$~~

~~122300~~

~~$$\begin{array}{r} 8 | \overline{723} \\ \underline{5} \quad \quad \quad 8 | 144 - 3 \\ \underline{3} \quad \quad \quad 5 | 28 - 4 \\ \underline{4} \quad \quad \quad 5 | 5 - 3 \\ \underline{2} \quad \quad \quad 5 | 2 - 0 \\ \underline{0} \quad \quad \quad 0 | 0 - 1 \end{array}$$

$0 \cdot 8 \times 8 = 4 \cdot 0$
 $0 \cdot 0 \times 8 = 0 \cdot 0$~~

$(10343.4000)_8$

Complements

- Reddish Complement (R 's complement)
- Diminished " $((R-1)^c - u)$

decimal - 10's complement
9's complement

Octal - 8's complement
7's "

~~Binary~~
Binary - 2's complement
1's "

Hexa - 16's
15's

If n is a positive number to the base γ with integer part of n digits then the γ 's complement of N is defined as $(\gamma^{n-1} - N)$.

$$(7634)_{10} = \gamma^n \Rightarrow n$$

$$n = 4$$

$$\gamma = 10$$

$$10^4 \text{ complement} = 10^4 - 7634 = 2366.$$

$$76.34$$

$$100 - 76.34$$

$$23.66$$

$(11011)_2$

$$\begin{array}{r}
 & \xrightarrow{2} \text{Want} \quad \underline{\underline{32}} \\
 2 & | \quad 32 \\
 2 & | \quad 16 \quad 0 \\
 2 & | \quad 8 \quad 0 \\
 2 & | \quad 4 \quad 0 \\
 2 & | \quad 2 \quad 0 \\
 2 & | \quad 1 \quad 0 \\
 2 & | \quad 0 \quad -1
 \end{array}$$

$$\begin{array}{r}
 0000000 \\
 - 0011011 \\
 \hline
 0000101
 \end{array}$$

 $(00101)_2$

$$\begin{array}{r}
 38516 \\
 1947 \\
 \hline
 1909
 \end{array}$$

If N is a no, base δ and n integers and δ^{n-1-m} fractional digits. Then δ^{-1} complement is or $(\delta^{n-m} - N)$ or $(\delta^{n-1} - N)$

Add 1 to $(\delta-1)$'s complement to get δ 's complement.

1 's complement + 1 = 2 's complement

Subtraction

Bunk Pages - The Social Notebook

Step 1 → Equate the no. of digits of both given no.'s, if they are not equal apply the padding of zeros to make them equal.

Step - 2 → Find 8's complement of ^{minuend}subtrahend, ^{minuend}not having minuend

Step 3 → Add ^{minuend} and ^{subtrahend}. If sum produces carry then discard carry. and if the sum does not produce any carry, take the 8's complement to the result of sum and place a -ve sign in front of it.

$$Q \rightarrow 765320 - 4250$$

$$\begin{array}{r} 765329 \\ \underline{- 4250} \\ 76532 \\ 04250 \end{array} \rightarrow \text{minuend}$$

~~765329~~
76532
04250 → subtrahend.

8's Complement of subtrahend.

$$10^5 - 04250$$

$$\Rightarrow 95750$$

$$\begin{array}{r} 95750 \\ 76532 \\ \hline \times 72282 \end{array}$$

$$04250 - 76532$$

10's comp. of 76532

$$10^5 - 76532$$

~~37578 28468~~

$$\begin{array}{r}
 9999 \\
 +00000 \\
 73532 \\
 \hline
 286418
 \end{array}$$

~~28468~~

~~04250~~

~~280718~~

\downarrow 10's comp.

$$10^5 - 27$$

$$\begin{array}{r}
 30718 \\
 -72282 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 1000000 \\
 29718 \\
 \hline
 72282
 \end{array}$$

11101-1100

2' com \rightarrow 01100


$$\begin{array}{r}
 10011 \\
 +1 \\
 \hline
 10100
 \end{array}$$

10100


11101

$$\begin{array}{r}
 + \\
 \textcircled{X}10001
 \end{array}$$

Binary Codes

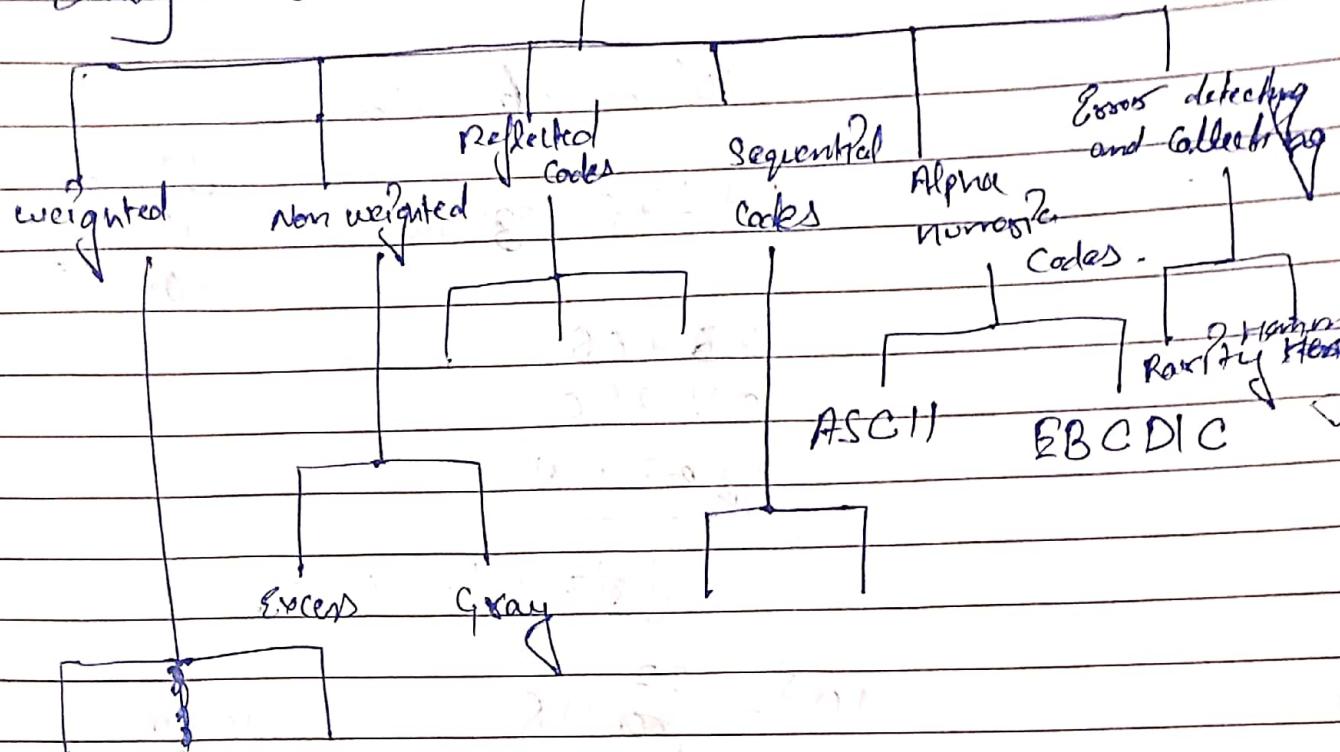

Binary BCD

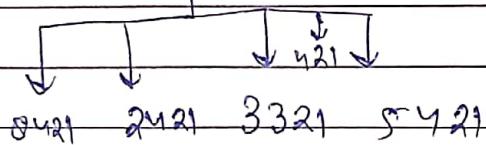

2 bit

2bit

1 0

0 1

1 0

1 1

3 bit

1 0

4 bit

1 0 1 0

~~8 → 3 bit~~

0 1 0

0 1 0

0 1 0

1 0 0

1 1 0

1 0 0

1 1 0

1 1 0

Digital systems are required to handle & manipulate data which may consist of alphabets or numerical. These alphabets, numbers or special characters are to be converted to binary format.

Weighted Codes :- In which each position of no. represents a specific wt. for 576

576
 ↓ ↗
 wt. of 100,
 wt. of 10.

Non weighted codes → Codes which are not assigned with any specific wt. to each digit position like Excess 3 or Gray codes

BCD addition :-

Step 1 → Add 2 BCD nos using ordinary binary addition.

Step 2 → If 4 bit sum = or less than 9 then no correction is needed the sum is in proper BCD form.

Step 3 → If the 4 bit sum is > 9 or if the carry is generated from the 4 bit sum then the sum is invalid. To correct this invalid sum

at 0110 to a 4 bit sum and
if there's any carry result from the addition
BCD add 8 to the next higher
digit.

$$\begin{array}{r} 175 \\ + 326 \\ \hline \end{array}$$

$$\begin{array}{r} 0001 & 0110 & 0101 \\ 0011 & 0010 & 0110 \\ + & \hline 0100 & 1001 & 1011 \end{array} \rightarrow \begin{array}{l} 7980 \\ \text{add 6.} \end{array}$$

$$\begin{array}{r} 0110 \\ \cancel{+ 29 \text{ add 6}} \\ \hline 0100 & 1010 & 0001 \\ + 1 & 0110 \\ \hline \end{array}$$

$\underbrace{0101}_5 \quad \underbrace{0000}_0 \quad \underbrace{0001}_1$

$$\begin{array}{r} 24 \\ 18 \\ \hline \end{array}$$

$$\begin{array}{r} 0010 & 0100 \\ 0001 & 1000 \\ + & \hline 0011 & 1100 \\ & | \\ & 0110 \\ \hline \end{array}$$

$\underbrace{0100}_{84} \quad \underbrace{0010}_{2}$

0 → 0 0 0 0 0 0
 1 → 0 0 0 0 1 1
 3 → 0 0 1 1 0 2
 2 → 0 0 1 0 0 3
 6 → 0 1 1 0 0 4
 7 → 0 1 1 1 0 5
~~5~~ → 0 1 0 1 0 6
 4 → 0 1 0 0 0 7
 12 → 1 1 0 0 0 8
 13 → 1 1 0 1 0 9
 15 → 1 1 1 1 0 10
 14 → 1 1 1 0 0 11
 10 → 1 0 1 0 0 12
 11 → 1 0 1 1 0 13
 9 → 1 0 0 1 0 14
 8 → 1 0 0 0 0 15

42 → 63

Error detecting and Correcting Codes

→ Hamming Codes → Parity

$N = m + P$
 ↴ no. of parity bits
 ↴ no. of msg. bits.
 → Total no. of bits in codes.

7	6	5	4	3	2	1
m_7	m_6	m_5	P_4	m_3	P_2	P_1
111	110	101	100	0011	010	001

When data is transmitted through a channel the noise generated by various sources existing in the channel corrupting it. So data can be recovered from the noise with the help of error detecting and correcting codes.

→ Hamming code is one of the codes used to find error and correcting it.

Parity bits - They are used to identify the error in the transmitted data. It is of two types odd parity and even parity.

odd parity - no. of 1's should be odd

even parity - no. of 1's should be even

10110 → odd parity

10111 → even parity

$$\boxed{m \leq 2^p - p - 1}$$

$$P = 2$$

~~$m \leq 2^2 - 2 - 1$~~

~~$4 \leq 1$~~

$$4 \leq 2^3 - 3 - 1$$

$$4 = 4$$

~~$m \leq 2^5 - 5 - 1$~~

~~$8 \leq 2^3 - 3 - 1$~~

~~(5)~~

1001

m_2	m_6	m_5	P_4	m_3	P_2	P_1	R
1	0	0	1	1	10	0	

$$P_1 \rightarrow 1, 3, 5, 7 \quad (1 \text{ at } 1^{\text{st}} \text{ position})$$

$$P_2 \rightarrow 2, 3, 6, 7 \quad (1 \text{ at } 2^{\text{nd}} \text{ position})$$

$$P_4 = 4, 5, 6, 7. \quad (1 \text{ at } 3^{\text{rd}} \text{ position})$$

$$P_1 \rightarrow 101\cancel{0}$$

$$P_2 \rightarrow 100\cancel{1}$$

$$P_3 \rightarrow 100\cancel{1}$$

1	0	0	1	1	0	0	0
			-	-			

Q → Assume the code word $100\underline{1}100$ is transmitted and $100\underline{0}100$ is received prove that the errors occurred and find out the correction bit if even parity is used.

m_2	m_6	m_5	P_4	m_3	P_2	P_1	R
11	110	101	100	011	010	001	
1	0	0	0	1	0	0	

$$P_1 \rightarrow 1, 3, 5, 7 \quad 1010 \leftarrow 0$$

$$P_2 \rightarrow 2, 3, 6, 7 \quad 1010 \leftarrow 0$$

$$P_3 \rightarrow 4, 5, 6, 7 \quad 1000 \times 1$$

100 → 4 bit is wrong

$m = 1101 / \text{odd parity}$.

m_7	m_6	m_5	P_4	P_7	mP_2	P_1
1	1	0	1	1	0	0
011	110	101	100	011	010	001
1	0	0	1	1	0	1

$P_1 \rightarrow 1, 3, 5, 7$

$P_2 \rightarrow 2, 3, 6, 7$

$P_8 \rightarrow 4, 5, 6, 7$.

1001101

$P_1 \rightarrow 1, 3, 5, 7 \rightarrow 1101 \quad \text{---} \quad 0$

$P_2 \rightarrow 0, 2, 3, 6, 7 \rightarrow 0101 \quad 1$

$P_8 \rightarrow 4, 5, 6, 7 \rightarrow 1001 \quad 1$

110 → 6 bit \rightarrow wrong

$P_8 \rightarrow 10101$

m_7	m_8	m_7	m_6	m_5	P_4	m_3	P_2	P_1
1	1	0	1	0	1	1	0	0
1001 0	1000 0	0111 1	110 0	0101 0	100 1	011 1	010 0	001 0

$$m_i = 2P - P_i$$

$$q =$$

$P_1 \rightarrow 1, 3, 5, 7, 8, 9 \quad 1$

$P_2 \rightarrow 2, 3, 5, 7, 8, 9 \quad 1$

$P_8 \rightarrow 4, 5, 6, 7, 8, 9 \quad 1$

$P_8 \rightarrow 8, 9 \quad 1$

1110

110101100

00 101100

$$\begin{array}{l}
 P_1 \rightarrow 0, 1, 1, 0, 0, 1 \rightarrow 0 \\
 P_2 \rightarrow 0, 1, 1, 1, 0, 0 \rightarrow 10 \\
 P_3 \rightarrow 1, 0, 1, 1, 0 \rightarrow 0 \\
 P_8 \rightarrow 0, 1 \rightarrow 1
 \end{array}$$

Boolean Algebra :-

$$A+0 = A$$

$$A+1 = 1$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

$$A + \bar{A} = 1$$

$$A(B+C) = AB + AC$$

$$A + BC = (A+B)(A+C)$$

$$\bar{\bar{A}} = A$$

1) Number system and their conversion.

2) Basic Arithmetic of no. systems

3) Binary Codes (BCD, Gray code, Excess 3, 8421)
(Hamming code)

4) BCD and excess 3 arithmetic

5) Basic gates and universal gates.

6) Implementation of Boolean functions using universal gates

7) K map upto 4 variables

Excess 3 \rightarrow Add 3 to BCD code.

Solving of Boolean expression using Boolean Algebra

Sum of Products :- (So P)

Product of Sums :- (Pos)

A	B	C	m	M
0	0	0	$\bar{A}\bar{B}\bar{C}$	$A+B+C$
0	0	1	$\bar{A}\bar{B}C$	$A+B+\bar{C}$
0	1	0	$\bar{A}B\bar{C}$	$A+\bar{B}+C$
0	1	1	$\bar{A}BC$	$A+\bar{B}+\bar{C}$
1	0	0	$A\bar{B}\bar{C}$	$\bar{A}+B+C$
1	0	1	$A\bar{B}C$	$\bar{A}+B+\bar{C}$
1	1	0	ABC	$\bar{A}+\bar{B}+\bar{C}$
1	1	1	ABC	$\bar{A}+\bar{B}+\bar{C}$

$$y = AB + BC + AC$$

$$y = AB(C+\bar{C}) + (A+\bar{A})BC + \bar{A}C(B+\bar{B})$$

$$y = ABC + AB\bar{C} + AB\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$y = ABC + \bar{A}BC + AB\bar{C}$$

$$y = \underset{111}{AB\bar{C}} + \underset{110}{AB\bar{C}} + \underset{010}{\bar{A}BC} + \underset{100}{\bar{A}B\bar{C}}$$

$$f(A,B,C) = \sum m(7, 6, 2, 4)$$

Encl	A	B	C	y	
0	0	0	0	1	$\sum m(0, 1, 3, 4, 6, 7)$
1	0	0	1	1	
2	0	1	0	0	$\sum m(2, 5)$
3	0	1	1	1	
4	1	0	0	1	$\sum \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$
5	1	0	1	0	$+ AB\bar{C} + ABC$
6	1	1	0	1	$\sum = (A+\bar{B}+C)(\bar{A}+B+\bar{C})$
7	1	1	1	1	$\sum = AB + AC + \bar{A}\bar{B} + BC + \bar{A}\bar{C} + AC$

$$\begin{aligned}
 & AB(C\bar{C}) + A\bar{C}(B\bar{B}) + \\
 & AB(C+\bar{C}) + A\bar{C}(B+\bar{B}) + \bar{A}\bar{B}(C+\bar{C}) + \bar{B}\bar{C}(A+\bar{A}) + \\
 & \bar{A}C(B+\bar{B}) + BC(A+\bar{A}) \\
 & AB + ABC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + (\bar{A}\bar{B}\bar{C}) + \\
 & \bar{A}BC + \bar{A}\bar{B}C + ABC + \bar{ABC} \\
 & ABC + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}C \\
 & 111 \quad 110 \quad 100 \quad 001 \quad 000 \quad 011 \\
 & 7 \quad 6 \quad 4 \quad 1 \quad 0 \quad 3
 \end{aligned}$$

$$\Sigma_m(0, 1, 3, 4, 6, 7)$$

This implies SOP & POS are complementary.

$$g \rightarrow \overline{AB} + \bar{A} + AB$$

$$\overline{(AB)} \quad A, (\overline{AB})$$

$$AB + \bar{A}C + A\bar{B}C \quad (AB + C)$$

$$AB + \bar{A}C + A\bar{B}C, \quad AB + A\bar{B}C, C$$

$$AB + \bar{A}C + A\bar{B}C,$$

$$A(B + \bar{B}C) + \bar{A}C$$

$$A((B+\bar{B})(B+C)) + \bar{A}C$$

$$AB + AC + \bar{A}C$$

$$\cancel{AB} \quad |$$


AB	$C+D=00$	$C+D=01$	$C+D=11$	$C+D=10$
$A+B=00$	X ₀	X ₁	X ₃	X ₂
$A+\bar{B}=01$	0 ₄	0 ₅	0 ₇	0 ₆
$\bar{A}+\bar{B}=11$	0 ₁₂	1 ₈	1 ₁₅	X ₁₄
$\bar{A}+B=10$	0 ₈	X ₉	X ₁₁	1 ₀

$(A+B)(C+D)$.

AB	$CD=00$	$CD=01$	$CD=11$	$CD=10$
$\bar{A}\bar{B}$	X ₀	1 ₁	1 ₃	X ₂
$\bar{A}B$	4	X ₅	1 ₇	6
AB	1 ₂	1 ₃	1 ₁₅	1 ₄
$A\bar{B}$	0	9	1 ₁₄	1 ₀

$\bar{A}\bar{B} + CD$
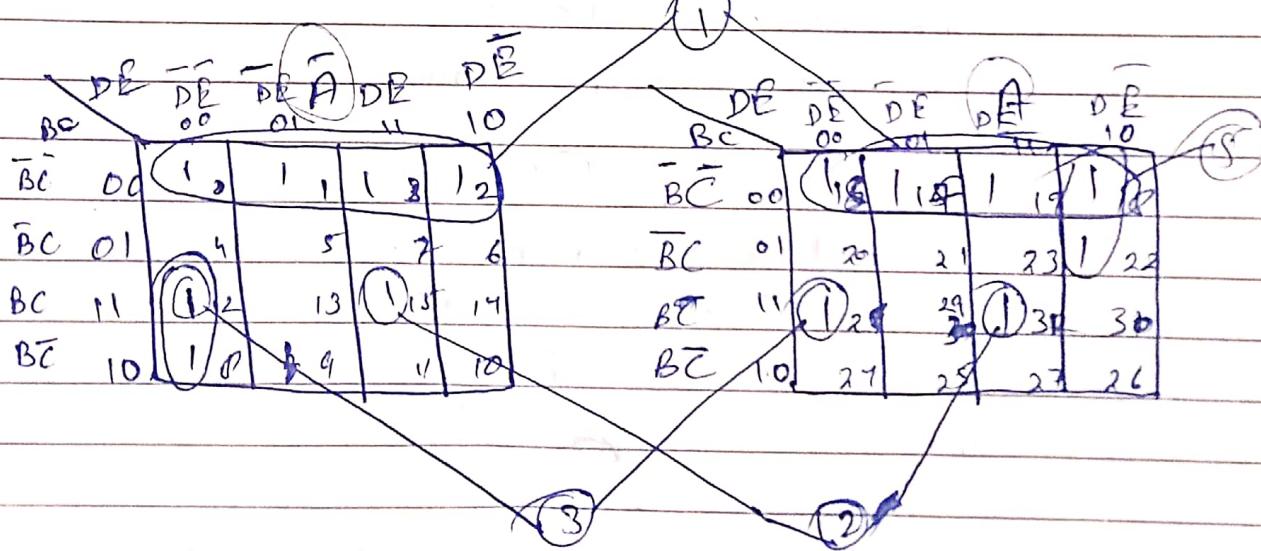
$$f(A, B, C, D, E) = \sum m(0, 1, 2, 3, 8, 12, 15, 16, 17, 18, 19, 23, \frac{20}{25}, 31)$$



$$f \rightarrow \bar{B}\bar{C} + \bar{A}B\bar{D}\bar{E} + BC\bar{D}B + BC\bar{D}\bar{B} + A\bar{B}D\bar{E}$$

$$\text{Q} \rightarrow S_m = \{0, 4, 8, 12, 15, 16, 17, 18, 19, 22, 23\},$$

$$S_m = \{0, 4, 8, 12, 16, 18, 20, 22\} \text{ and } \{24, 26, 28, 30, 31\}.$$

	$\bar{B}C$	$D\bar{E}$	$\bar{D}\bar{E}$	$\bar{D}A$	$D\bar{E}$	$D\bar{E}$	$\bar{B}C$	$D\bar{E}$	$\bar{D}\bar{E}$	$\bar{D}A$	
$\bar{B}C$	00	11	00	1	3	2	00	11	16	19	18
$\bar{B}C$	01	10		5	7	6	01	10	20	21	23
$\bar{B}C$	11	11	10	13	15	14	11	X	28	29	X
$\bar{B}C$	10	10	01	9	11	10	10	X	21	28	X

$\bar{D}\bar{E}$ + $A\bar{D}\bar{E}$

$\bar{D} + (\bar{D} + \bar{A}\bar{D})$

$\bar{D}((A + \bar{D}))$

$\bar{D}\bar{D} + A\bar{D}$

∴ Nine MC Clukey method (Tabulation method)

Step 1 → write all the minterms in their equivalent binary form.

Step 2 → arrange the minterms based on the no. of 1's.

Step 3 → Compare each binary no. from 1 group to another and if they differ only by 1 bit position put -/ mask and copy the remaining term. and place ✓ after each comparison

At step 4 → Apply the same process described in Step 3 for the resultant column and continue the cycles until a single pass through cycle yields no further

elimination.

- Step-5- list all the uncheck prime implicants and form a prime implication chart. Each prime implicant is represented in a row and each minterm in a column. The cross mark are placed in each row to show the comparison of minterm that makes a prime implicant
- search for single cross mark column and select the prime implicant corresponding to that.
 - search for multiple dot columns step one by one & if the corresponding minterm is already included in the final expression, ignore the minterm and go to next multiple column. otherwise include the corresponding prime implicant in the final expression.

$$F(A, B, C, D) = \Sigma m(0, 1, 3, 6, 7, 8, 10, 12, 13)$$

0000, 0010, 0011, 00110, 0111, 1000, 1010, 1100, 1101
 $m_0 \quad m_2 \quad m_3 \quad m_6 \quad m_7 \quad m_8 \quad m_0 \quad m_{12} \quad m_{13}$

\bar{m}_0	0000		00-0 (0, 2)		
\bar{m}_2	0010		-000 (0, 8)		
\bar{m}_3	1000		001- (2, 3)		discarded 2 bit
\bar{m}_6	0011		0-10 (2, 6)		change
\bar{m}_7	0110		-010 (2, 10)		
\bar{m}_8	1010		10-0 (0, 10)		
\bar{m}_{12}	1100		1-00 (8, 12)		
\bar{m}_9	0111				
\bar{m}_{13}	1101				

$$0-11, (3, 7)$$

$$011-, (6, 7)$$

$$110-, (12, 13)$$

~~$$00-0(0,2)$$~~

~~$$-000(0,8)$$~~

~~$$001-(2,3)$$~~

~~$$10-10(3,6)$$~~

~~$$1-010(1,10)$$~~

~~$$10-0(0,10)$$~~

~~$$*1-00(0,12)$$~~

~~$$0-11(13,7)$$~~

~~$$1011-(16,7)$$~~

~~$$*110-(12,13)$$~~

A B C D

$$\bar{A}, \bar{B} - \bar{D} \quad (0, 2, 8, 10)$$

$$- \bar{A} - \bar{D} \quad (0, 8, 2, 10)$$

$$0 - 1 - \quad (2, 3, 6, 7)$$

$$- \bar{A} - 1 - \quad (2, 6, 3, 7)$$

$$\bar{B} \bar{D} \quad (0, 2, 8, 10)$$

$$\bar{A} C \quad (2, 3, 6, 7)$$

prime implicants

$$\bar{B} \bar{D} \quad (0, 2, 8, 10)$$

$$\bar{A} C \quad (2, 3, 6, 7)$$

$$A \bar{C} \bar{D} \quad (0, 12)$$


$$A B \bar{C} \quad (12, 13)$$

	0	2	3	6	7	8	10	12	13
$\bar{B} \bar{D}$	X	X				X	X		
$\bar{A} C$		X	X	X	X				
$A \bar{C} \bar{D}$				X		X		X	
$A B \bar{C}$						X		X	X

$$AB\bar{C} + \bar{B}\bar{D} + \bar{A}C + \bar{B}\bar{D}$$

$$AB\bar{C} + \bar{B}\bar{D} + \bar{A}C$$

→ Some literals agree.

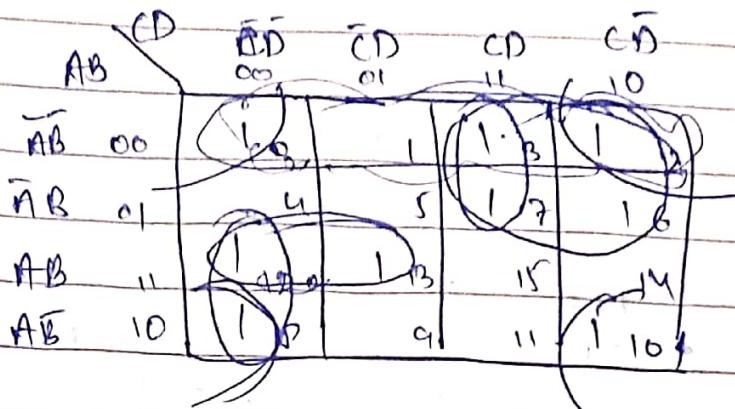

$$\bar{A}\bar{B} + \bar{A}CD + A\bar{B}\bar{D} + ABC$$

~~$$\bar{A}\bar{B} + \bar{A}C + AB\bar{C} + \bar{B}\bar{D}$$~~

$$g \rightarrow f = \sum m(0, 1, 9, 15, 24, 29, 30) + d(0, 11, 31)$$

$$g \rightarrow \sum m(1, 3, 7, 11, 15) + d(0, 10, 2, 5)$$


	0 0 0	(0, 1) -	A B C D	AB
m_0	0 0 0 1	0 0 - 0	0 0 - -	$\{0, 1, 2, 3\}$
m_1	0 0 1 1	0 0 - 1	0 0 - -	$\{0, 2, 1, 3\}$
m_3	0 1 1 1	0 - 0 1	0 - - 0 1	$\{1, 3, 5, 7\}$
m_7	1 0 1 1	0 0 1 -	0 - - 1	$\{2, 4, 5, 3, 7\}$
m_{11}	1 0 0 1	0 - 1 1	- - 1 1	$\{3, 7, 11, 15\}$
m_{15}	1 1 1 1	- 0 1 1		
\bar{m}_7	0 1 1 1	0 1 - 1		
\bar{m}_{11}	1 0 1 1	- 1 1 1		
\bar{m}_{15}	1 1 1 1	1 - 1 1		

Prime Implicant	0	1	3	7	15	29	30	8	14	31
$\bar{A}\bar{B}$	X	X				X	X			
$\bar{A}D$	X	X	X					X		
CD	X	X	(X)	(X)					X	

~~$$\bar{A}D + CD$$~~

All no's must be included if not ~~rept~~ well the
don't care. then.
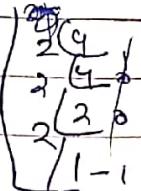
$$\{6, 0, 1, 9, 15, 24, 29, 30\} + d(0, 1, \frac{31}{15})$$





00009, 00001, 01001, 01111, 11000, 11101, 11110 01000, 6(011, ~~112~~(8)
0 1 4 15 24 29 30 8 11 31 27-1

m_{18}	$m_{18} 00000$	$0000 - \underline{10,11}$	$-$	$0 - 00 - (0, 18, 24)$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 3-1 \\ 2-1 \\ 2-1 \\ 2-1 \end{smallmatrix}$
m_{19}	$m_{19} 00001$	$0 - 000 \quad (0, 8)$	$-$	$0 - 00 - (0, 8, 1, 9)$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-1 \\ 2-1 \\ 2-1 \\ 2-1 \end{smallmatrix}$
m_{20}	$m_{20} 01000$	$0 - 001 \quad (1, 9)$	$-$	$-$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-0 \\ 2-0 \\ 2-0 \\ 2-0 \end{smallmatrix}$
m_{21}	$m_{21} 01001$	$0100 - (8, 9)$	$/$	$-$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-0 \\ 2-0 \\ 2-0 \\ 2-0 \end{smallmatrix}$
m_{22}	$m_{22} 11000$	$-1000 \quad (8, 24)$	$.$	$-$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-0 \\ 2-0 \\ 2-0 \\ 2-0 \end{smallmatrix}$
m_{23}	$m_{23} 01011$	$010 - \underline{1(9,11)}$	$-$	$01 - 11 \quad (11, 18)$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-1 \\ 2-1 \\ 2-1 \\ 2-1 \end{smallmatrix}$
m_{24}	$m_{24} 11110$	$1111 \quad \underline{0} \quad (30, 31)$	$.$	$-$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-1 \\ 2-1 \\ 2-1 \\ 2-1 \end{smallmatrix}$
m_{25}	$m_{25} 01111$	$-1111 \quad (15, 31)$	$-$	$-$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-1 \\ 2-1 \\ 2-1 \\ 2-1 \end{smallmatrix}$
m_{26}	$m_{26} 11111$	$01 - 1 \quad (29, 31)$	$-$	$-$	$\begin{smallmatrix} 2 \\ 2 \\ 2 \\ 2 \end{smallmatrix}$	$\begin{smallmatrix} 2-1 \\ 2-1 \\ 2-1 \\ 2-1 \end{smallmatrix}$

prime implicant	0	1	9	15	24	29	30	8	11	31
ABC		X	X						X	
$B\bar{C}\bar{D}\bar{E}$					X	X			X	
$A\bar{B}C\bar{F}$				X						X
ABDE					X					X
ABCD								X		X
$\bar{B}C\bar{D}B$					X					X
ABC \bar{F}						X				X

$$ABC + A\bar{B}CE + ABCD + BCDE + A\bar{B}DE$$

Binary Parallel Adder :-

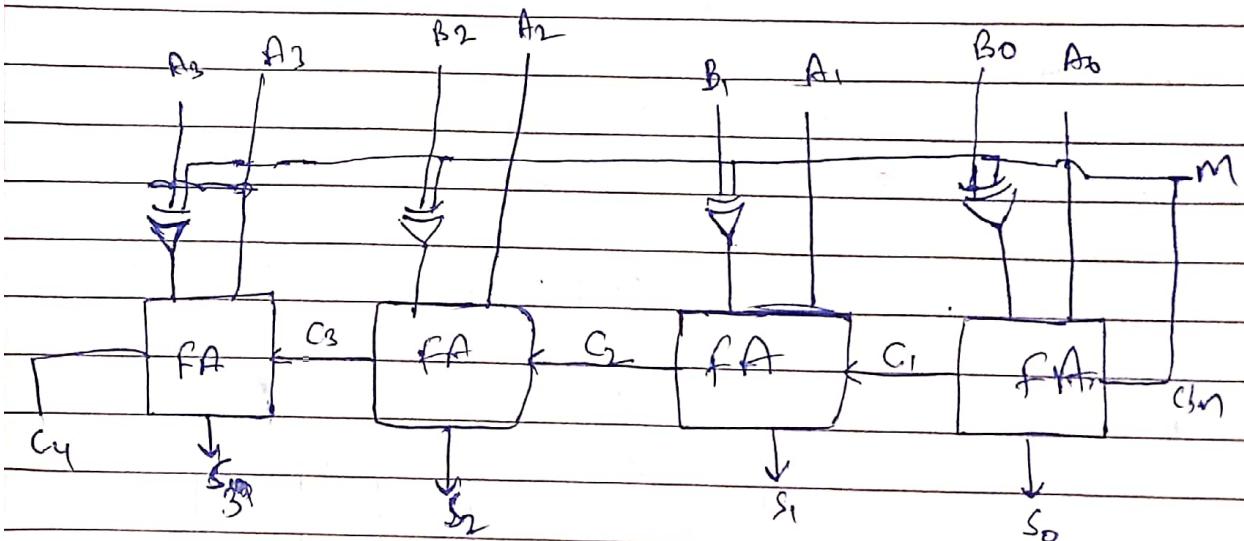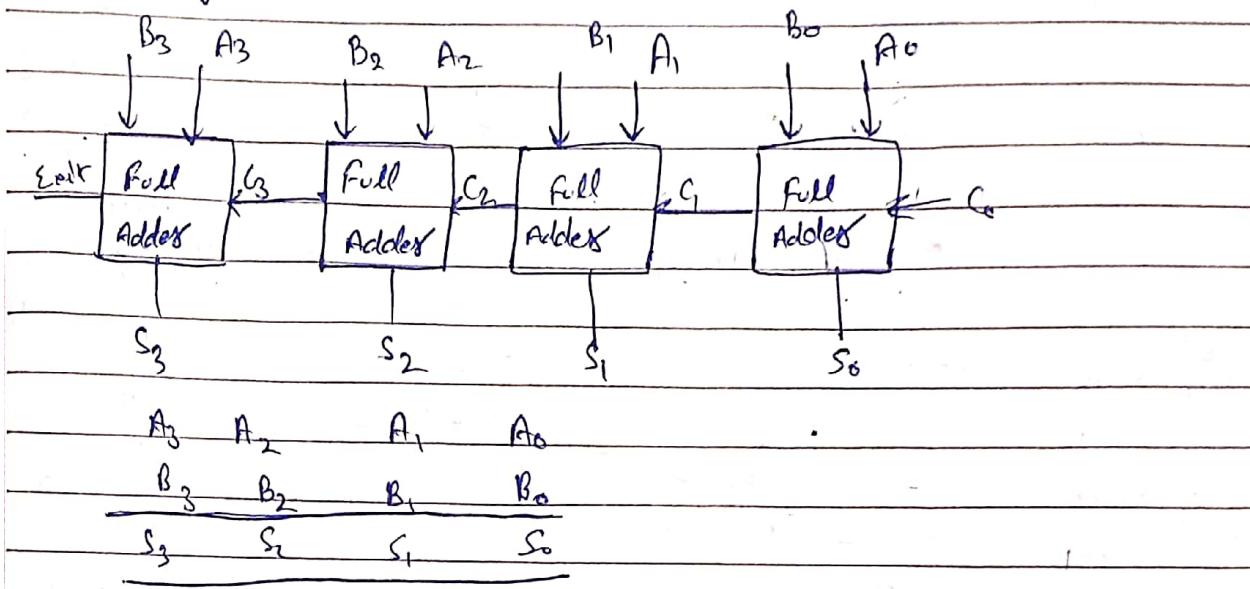

If $m = 0$ circuit is adder.




If $m = 1$ circuit is subtractor.

BCD Adder :-

s_3	s_2	s_1	s_0	y
0	0	0	0	0
1	0	0	0	0
2	0	0	1	0
3	0	0	1	0
4	0	1	0	0
5	0	1	0	0
6	0	1	1	0
7	0	1	1	0
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1


$s_3 s_2$	$s_3 s_0$	$s_2 s_0$
00	0	1
01	1	0
10	1	1
11	1	1

$$s_3 s_2 + s_3 s_1$$

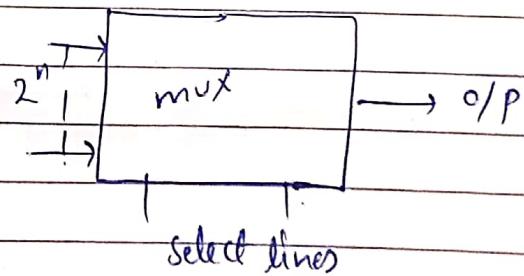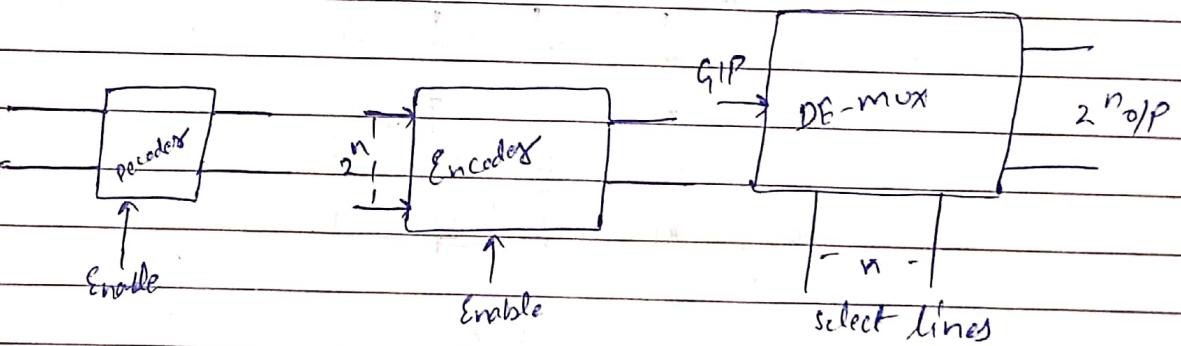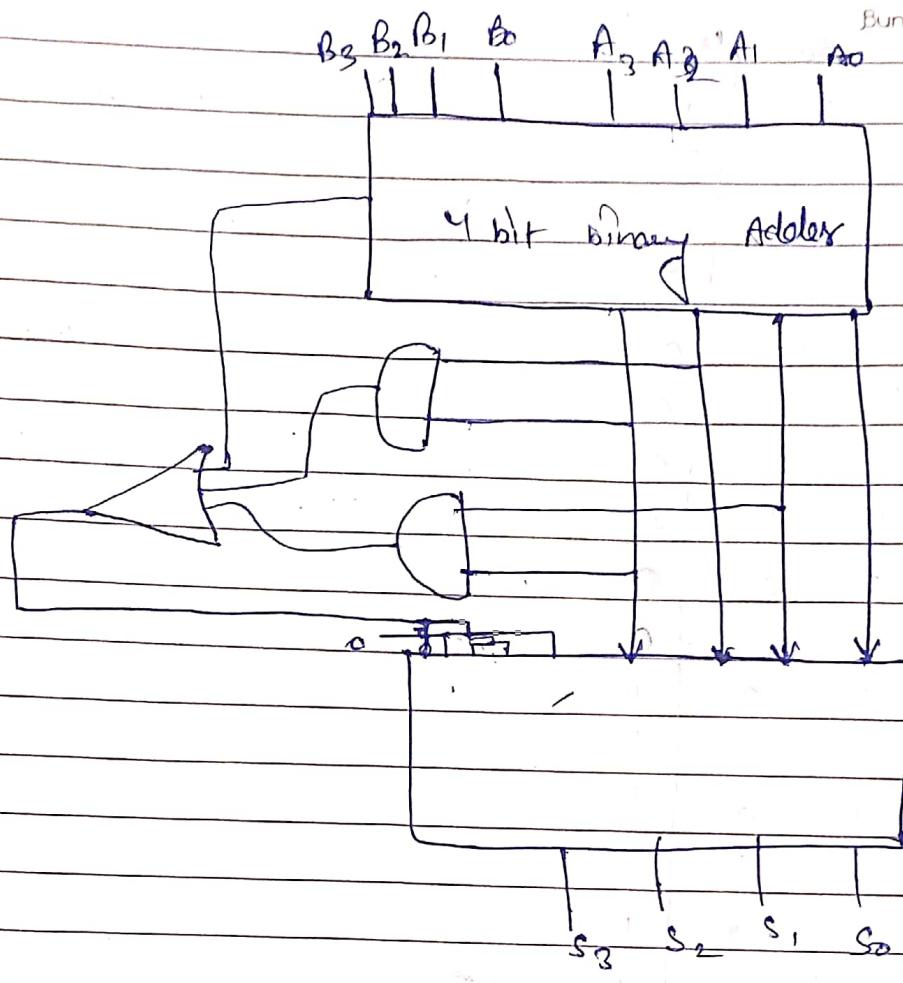


MULTIPLEXER

Bunk Pages - The Social Notebook

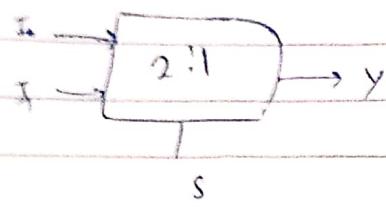

$$\begin{array}{ll} S=0 & Y = I_0 \\ S=1 & Y = I_1 \end{array}$$

$$Y = \bar{S}I_0 + SI_1$$


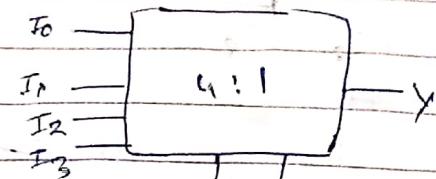




S ₁	S ₀	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

$$S = \bar{I}_0 \rightarrow \bar{S}I_0 + SI_1$$

$$S = \bar{S}_1\bar{S}_0I_0 + \bar{S}_1S_0I_1 + S_1\bar{S}_0I_2 + S_1S_0I_3$$

$$S = I_0 +$$

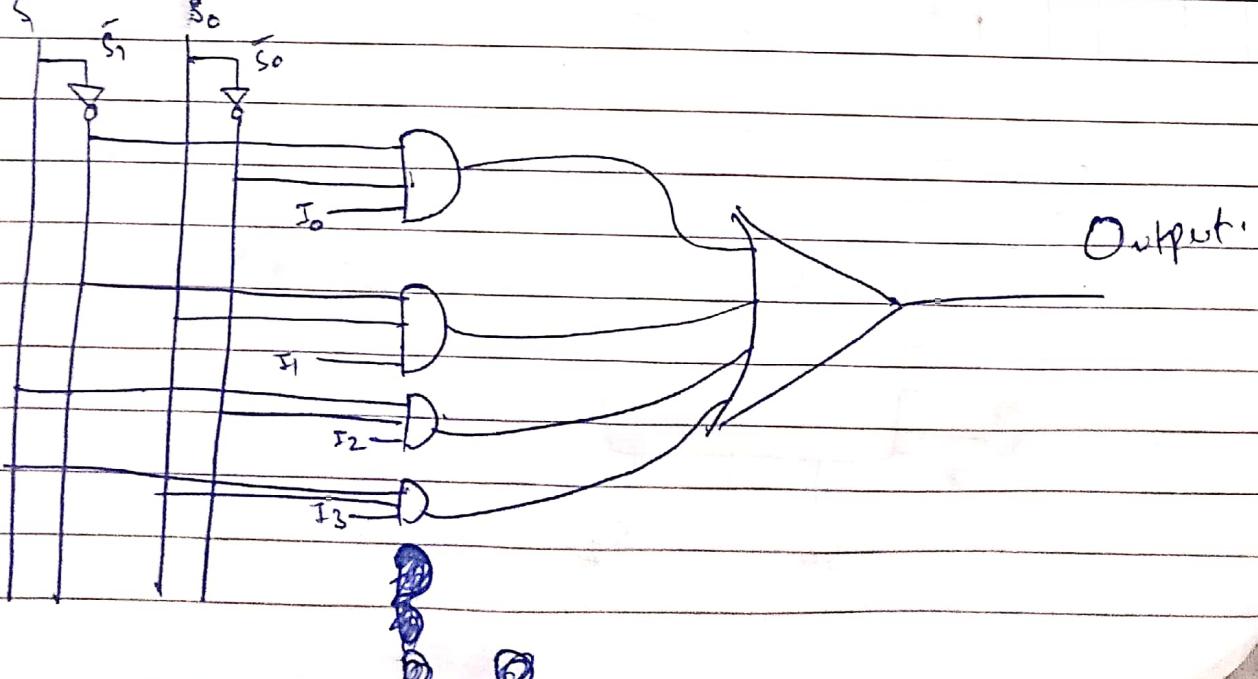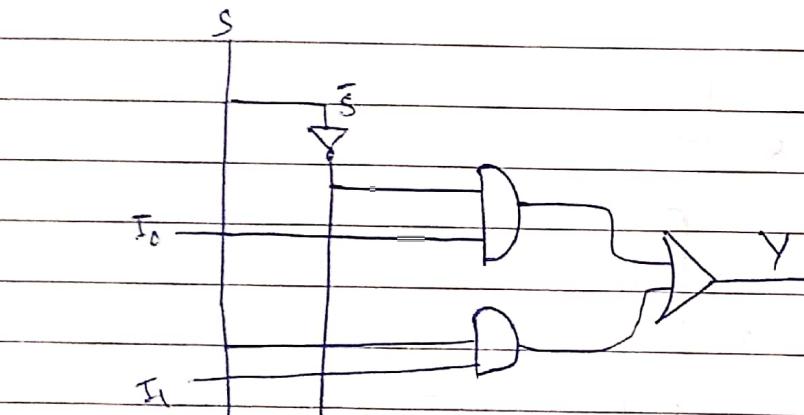


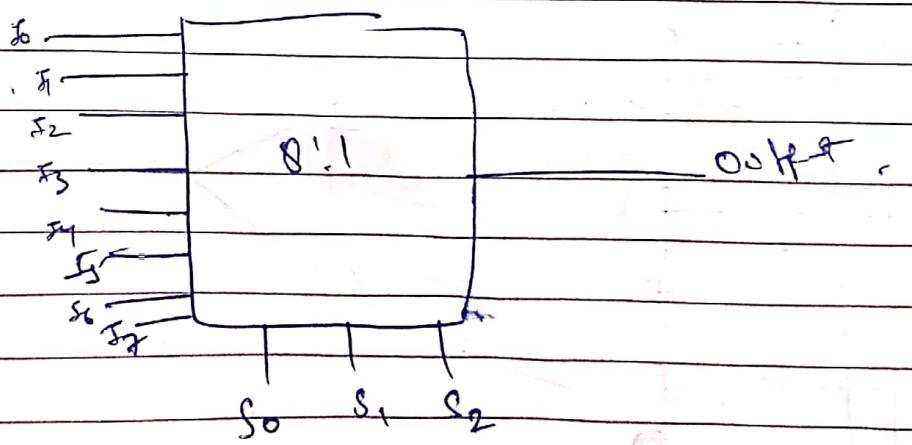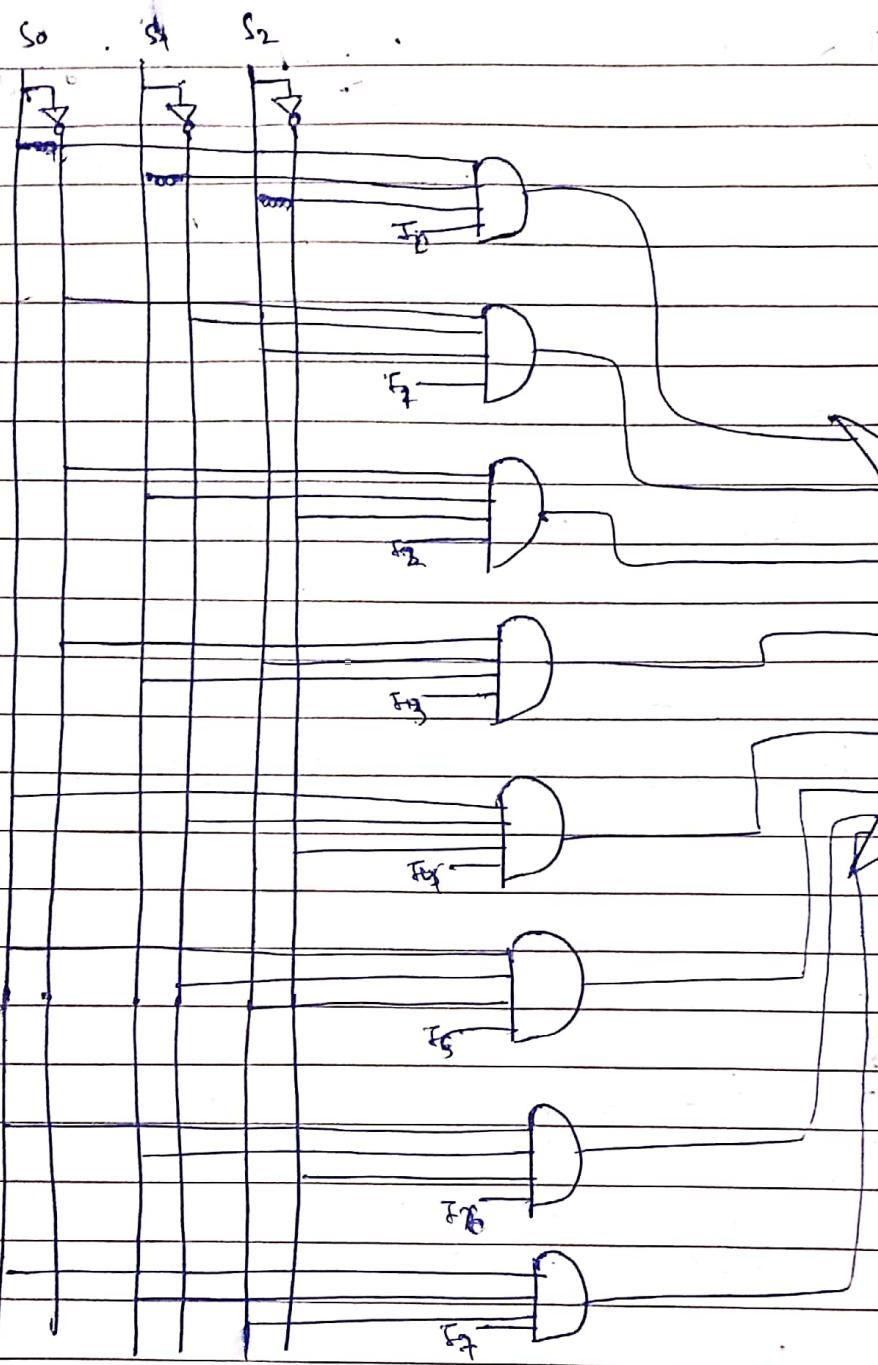

S_0	S_1	S_2	Output
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

$$Y = \bar{S}_0 \bar{S}_1 \bar{S}_2 I_0 + \bar{S}_0 \bar{S}_1 S_2 I_1 + \dots$$

Q → 8.1 using $2 \times (4:1)$.

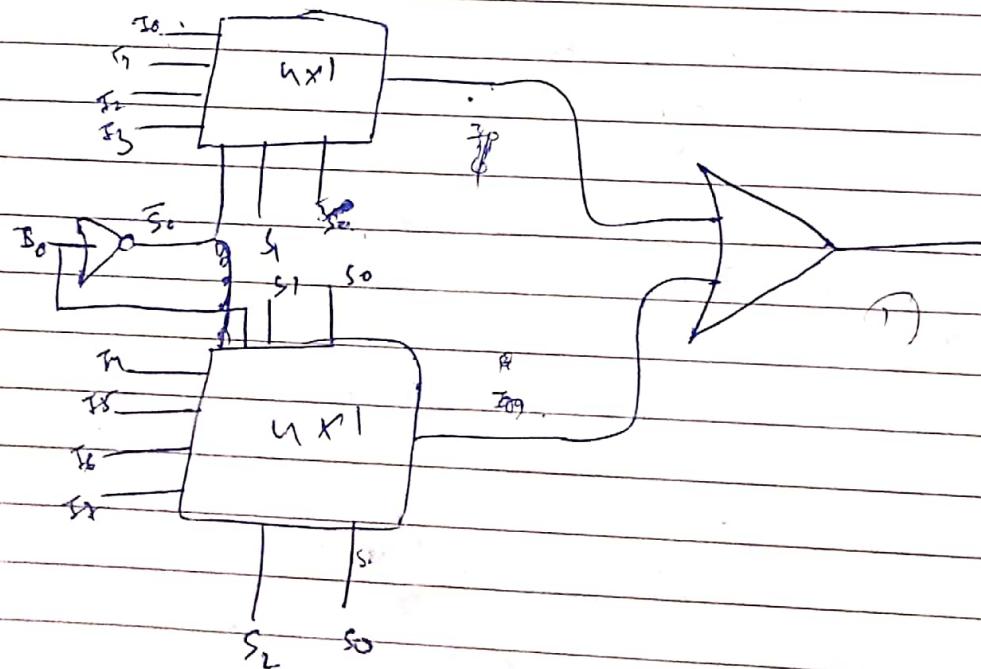


1 bit Comparator

A	B	$A < B$	$A > B$	$A = B$	
0	0	0	0	1	
0	1	1	0	0	
1	0	0	1	0	
1	1	0	0	1	

$$x = \bar{A}B$$

$$y = A\bar{B}$$

$$z = \bar{A}\bar{B} + AB + A\oplus B$$

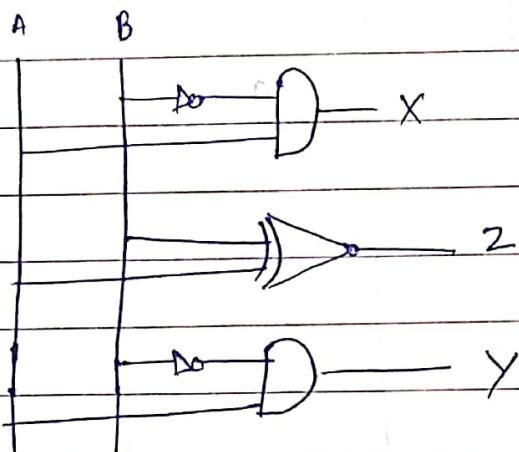

A_1	A_0	B_1	B_0	$X = A \wedge B$	$Y = A \geq B$	$Z = ^* A = B$	
0	0	0	0	0	0	1	
1	0	0	1	1	0	0	
2	0	0	1	0	1	0	
3	0	0	1	1	1	0	
4	0	1	0	0	0	1	
5	0	1	0	1	0	0	
6	0	1	1	0	1	0	
7	0	1	1	1	1	0	
8	1	0	0	0	0	0	
9	1	0	1	1	0	1	
10	1	0	1	0	0	0	
11	1	0	1	1	1	0	
12	1	1	0	0	0	1	
13	1	1	0	1	0	1	✓
14	1	1	1	0	0	1	0
15	1	1	1	1	0	0	

$$\textcircled{1} \quad Z = (A_1 \odot B_1) \cdot (A_0 \odot B_0)$$

$$X = \bar{A}_1 B_1 + (A_1 \odot B_1) \cdot \bar{A}_0 B_0$$


$$Y = A_1 \bar{B}_1 + (A_1 \odot B_1) A_0 \bar{B}_0$$

$A_1 A_0$	\overline{B}_0	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
00	00	11	11	12	10
01	01	4	5	17	16
11	11	12	13	15	14
10	10	0	9	11	10

$$\bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

(A₁B₁)A₀
AB + AB

Bunk Paper - The Social Notebook

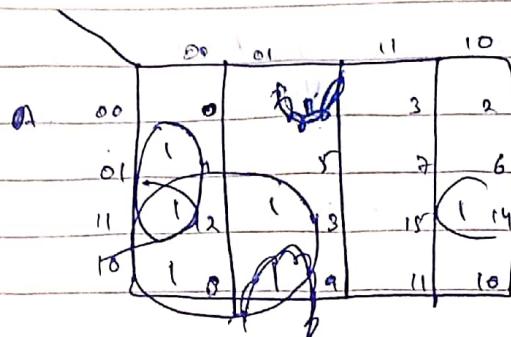


$$\bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 \bar{B}_0 (B_1 + \bar{B}_0)$$

$$A_1 \bar{B}_1 + \cancel{\bar{A}_0 \bar{B}_1 B_0} + \cancel{\bar{A}_0 \bar{B}_1 B_0} \\ + A_1 A_0 B_0$$

$$Y_2 = A_1 \bar{B}_1 + (A_1 \bar{B}_0) A_0 \bar{B}_0$$

$$\begin{aligned} & A_0 \bar{B}_1 + A_1 A_0 \bar{B}_0 \\ & A_0 (\bar{B}_1 + A_1 \bar{B}_0) \\ & A_0 ((\bar{B}_1 + A_1) (\bar{B}_0 + A_0)) \end{aligned}$$


$\bar{B}_1 B_0$

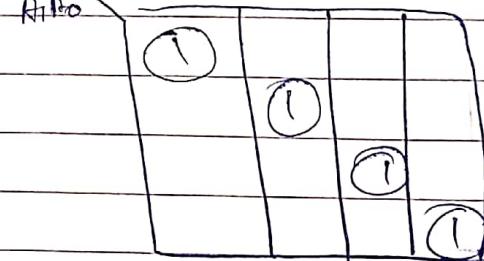


$$A_1 \bar{B}_1 +$$

$$\begin{aligned} & A_0 \bar{B}_1 + A_1 A_0 B_0 \\ & A_0 \bar{B}_0 \end{aligned}$$
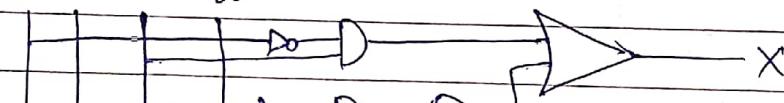
$$Z = (A_1 \bar{B}_1) \cdot (A_1 A_0 B_0)$$



$$Z = A_1 \bar{B}_1 B_0$$

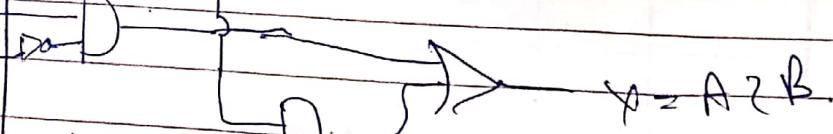


$$Y = A_1 B_1$$

Lecture 9
Implementation of boolean function using multiplexers.


$$F(A, B, C) = \Sigma m(0, 1, 3, 5, 7)$$


logic 1

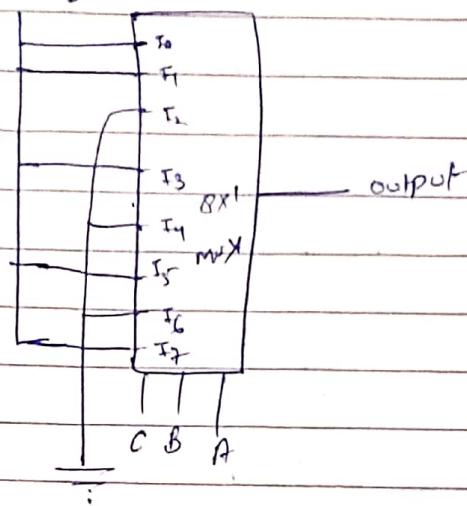

$$\Rightarrow F(A, B, C, D) = \Sigma m(0, 1, 3, 4, 7, 8, 9, 10, 14, 15)$$

16x1 8x1 4x1 2x1

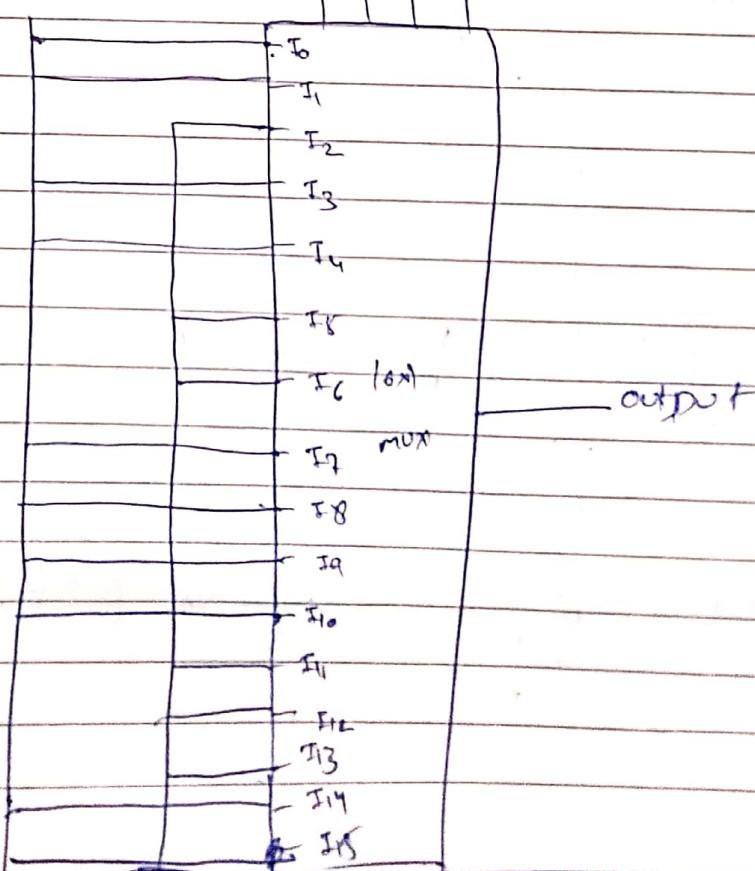

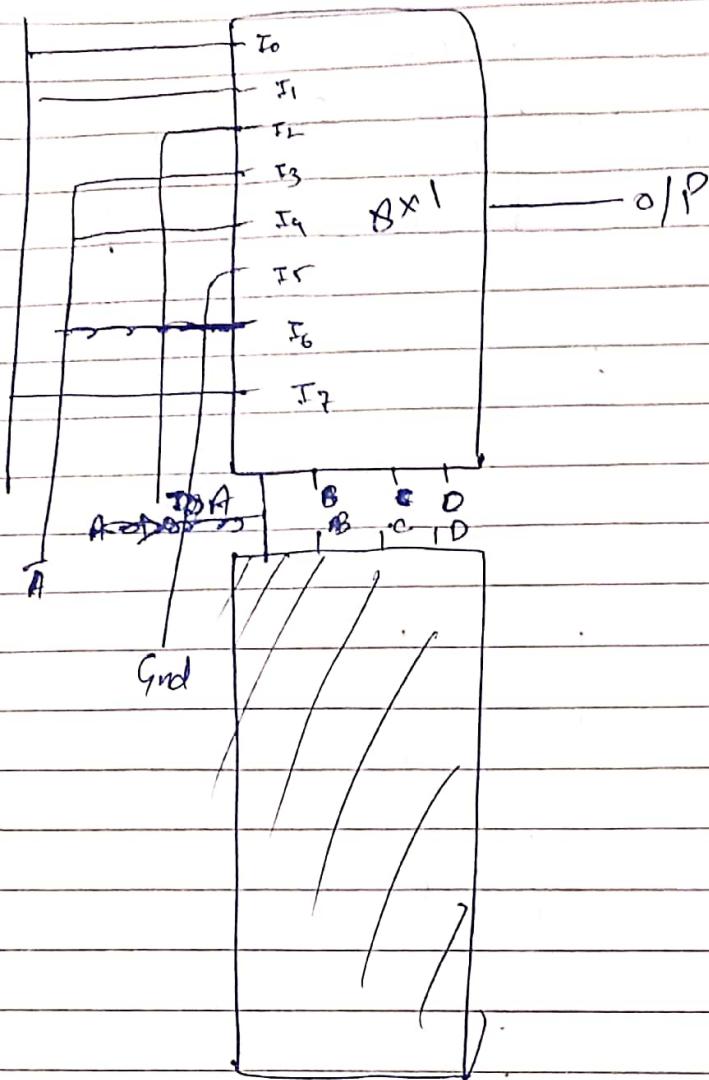


	000	001	010	011	100	101	110	111
0 A	(0)	(1)	2	(3)	(4)	5	6	(7)
1 A	(8)	(9)	(10)	11	12	13	(14)	(15)
	1	1	A	A	O	A	1	

Q4 Calc. using B as variable.

B	(0)	(1)	2	(3)	(8)	(9)	(10)	(11)
B	(4)	5	6	(7)	12	13	(14)	(15)
	1	B	O	1	B	B	1	B

$\phi \rightarrow$ Take C as a variable.

\bar{C}	(0)	(1)	(2)	5	(8)	(9)	12	13
C	2	3	6	7	10	11	14	15
	\bar{C}	1	\bar{C}	C	1	\bar{C}	C	C

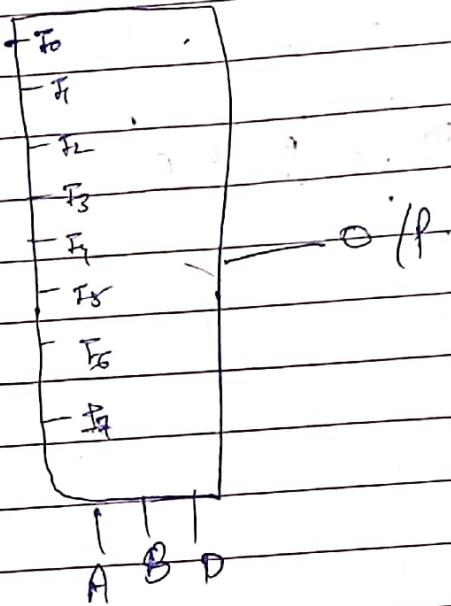


$\phi \rightarrow$ UXL.

	CD	$\bar{C}D$	$\bar{C}\bar{D}$	D	\bar{D}
$\bar{A}\bar{B}$ 00	(0)	(1)	2	(3)	
$\bar{A}\bar{B}$ 01	(4)	5	6	(7)	
$\bar{A}\bar{B}$ 10	(8)	(9)	(10)	11	
$\bar{A}\bar{B}$ 11	12	13	(14)	(15)	

$$\bar{A} + \bar{B} = (\bar{A} + \bar{B})(\bar{A} + B) = \bar{A} + B$$

$$\bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB = A + AB$$

$$\bar{A} + B$$

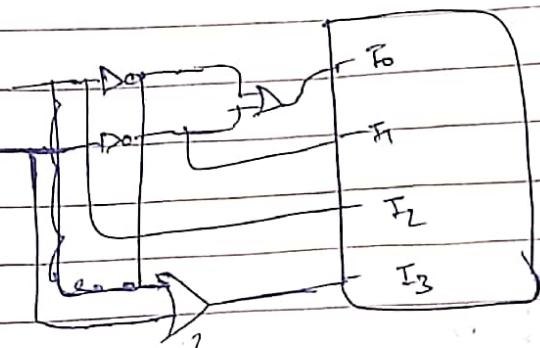

$\bar{A} \bar{B} \bar{C}$	000	0	2	0000	0	1	0
$\bar{A} \bar{B} C$	001	1	3	0001	2	3	1
$\bar{A} \bar{B} \bar{C}$	010	4	6	010	4	5	2
$\bar{A} \bar{B} C$	001	5	7	011	6	7	3
$A \bar{B} \bar{C}$	100	8	10	100	8	9	4
$A \bar{B} C$	101	9	11	101	10	11	5
$A \bar{B} \bar{C}$	110	12	14	110	12	13	6
ABC	111	13	15	111	14	15	7

$\bar{A} \bar{B} \bar{C}$	000	BC	BC	BC	BC
$\bar{A} \bar{B} C$	001	01	11	10	
$\bar{A} B \bar{C}$	010	10	10	10	

$$\bar{A} \bar{C} + \bar{A} C + A \bar{C}$$

\bar{A}	BC	$\bar{B}C$	BC	BC	$B\bar{C}$
0	00	01	11	10	
1	10	11	11	10	

$1 \quad 1 \quad 1 \quad 1$

$$\bar{B} \bar{C} + C + A \bar{B}$$

$$B \bar{C} + \bar{A} \bar{B} + BC$$

De-mux



1x14

1 x 8

1x16

n - selected lines


E	S_1	S_0	γ_0	γ_1	γ_2	γ_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


$$Y_0 = \bar{s}_1 \bar{s}_0 J$$

$$y_1 = \overline{s}_1 s_0 \cdot \overline{t}$$

$$\gamma_2 = s_1 \bar{s}_0 T$$

$$Y_3 = S_1 S_0 I$$

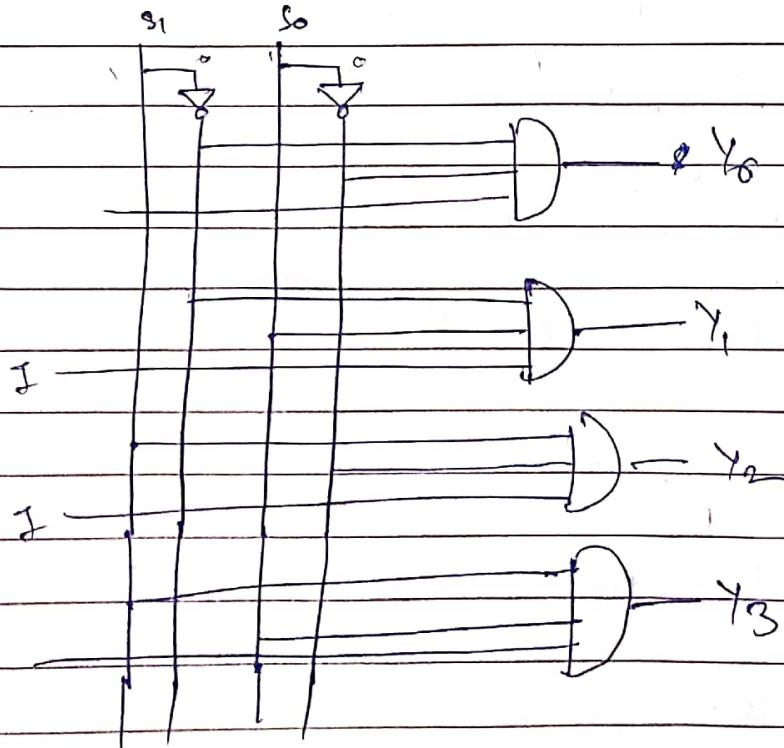

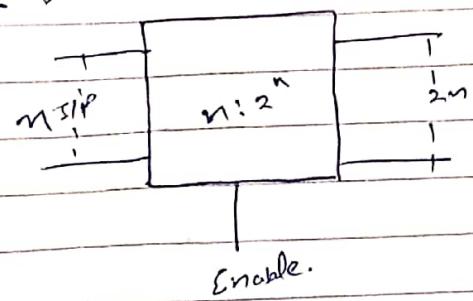Decoder :-


E	A	B	y_3	y_2	y_1	y_0
0	x	x	x	x	x	x
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

328

E	A	B	C	y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0
0	x	0	x	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0

BCD to 7 segment Converter


Bunk Pages - The Social Notebook

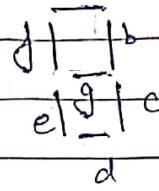

	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1


0 → abcdef
1 → bc
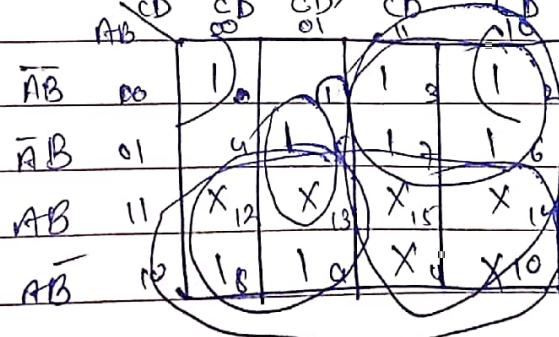
$$a = \sum m(0, 2, 3, 8, 6, 7, 8, 9) + d(10, 11, 13, 13, 14, 15)$$



$$\bar{A}C + A\bar{C} + A\bar{B}\bar{D}$$


$$A + C + BD + \bar{B}\bar{D}$$

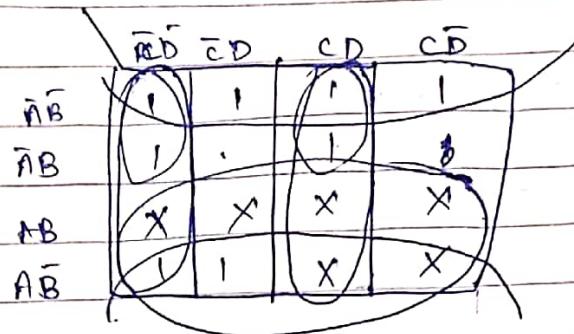

$$A + \bar{B} + \overline{AC\bar{D}} + \overline{ACD} = \bar{C}\bar{D} + CD$$

Encoder :-

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1



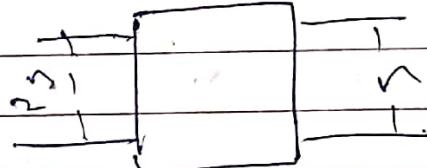


Enable Signal.

X X Y






$$A \rightarrow D_4 + D_5 + D_6 + D_7$$

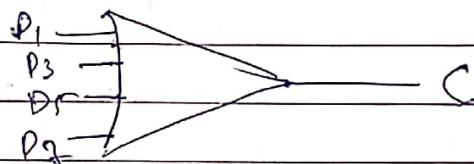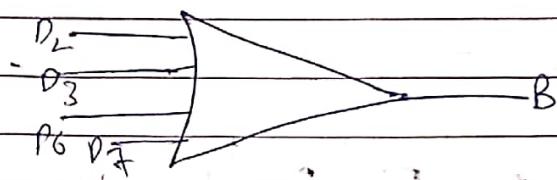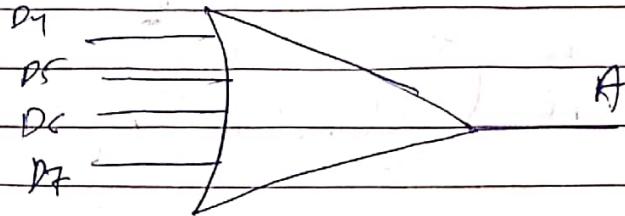

Priority Encoder \rightarrow If two or more inputs are equal to 1 at the same time then Input having the highest priority will be taken for the corresponding output.


D ₀	D ₁	D ₂	D ₃	Y ₀	Y ₁	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	1	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

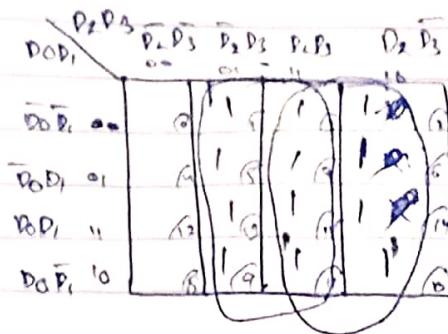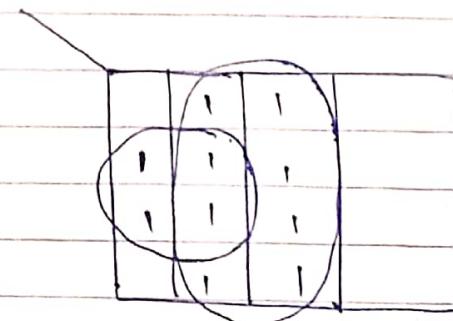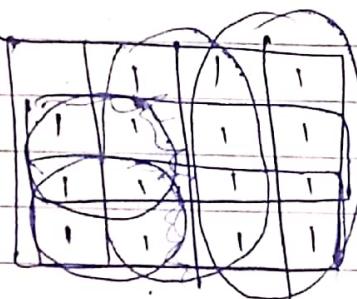 y_0 $D_3 + D_2$  y_1 $P_1 D_2 + D_3$  \sim $P_1 D_2 + D_3 + D_4 + D_2$ $D_2 + P_3 + P_1 + D_0$


Code Converter :-

Binary to BCD :-

A	B	C	D	\bar{B}_3	\bar{B}_2	\bar{B}_1	\bar{B}_0
0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	1
2	0	0	1	0	0	1	0
3	0	0	1	1	0	0	1
4	0	1	0	0	1	0	0
5	0	1	0	1	0	1	0
6	0	1	1	0	1	1	0
7	0	1	1	1	0	1	1
8	1	0	0	0	1	0	0
9	1	0	0	1	1	0	1
10	1	0	1	0	1	0	0
11	1	0	1	1	0	0	1
12	1	1	0	0	1	0	0
13	1	1	0	1	0	1	1
14	1	1	1	0	1	1	0
15	1	1	1	1	0	1	1

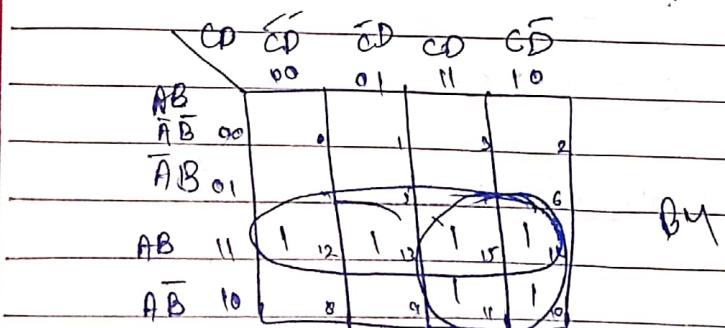


AB + AC

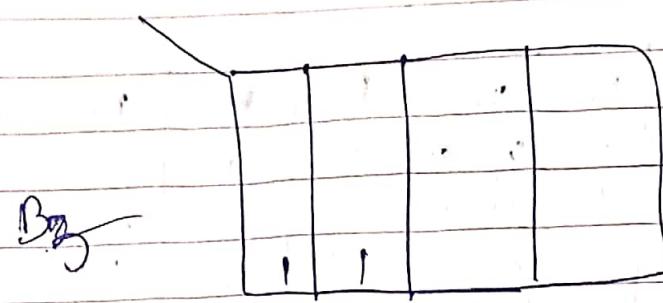

B₁


ĀB̄C̄

B₂

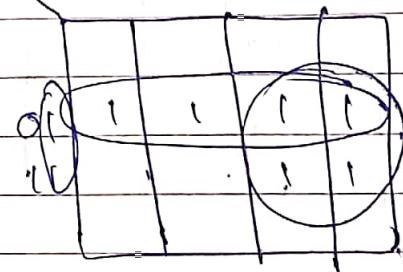


ĀB + B̄C

B₃

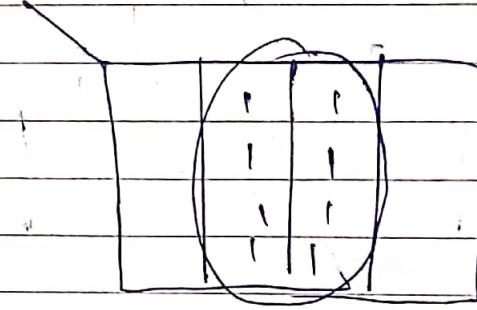

D

B₄

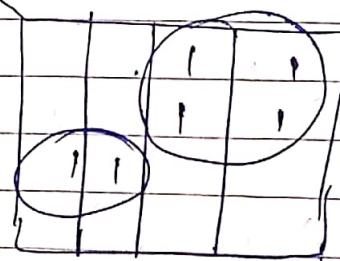

ĀB̄C̄ + ĀC̄

BCD to Excess 3.

	A	B	C	D	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	0	0	0
2	0	0	1	0	0	0	1	0
3	0	0	1	1	0	0	1	0
4	0	0	1	0	0	0	1	1
5	0	0	1	0	1	0	0	0
6	0	0	1	1	0	1	0	0
7	0	0	1	1	1	0	1	0
8	0	1	0	0	0	1	0	1
9	1	0	0	1	0	1	0	0

	CD	$\bar{C}D$	$\bar{C}\bar{D}$	$C\bar{D}$	$C\bar{D}$
B_3	00	•	•	•	•
	01	•	1	1	1
	11	X	X	X	X
	10	1	1	X	X


 $BD + BC + A$

$$\bar{ABC} + ABD + \bar{ABC}$$


B_2	00	01	11	11	1
	01	(1)	11	11	1
	11	X	X	X	X
	10	1	1	X	X

$$\bar{B}\bar{C}D + ABD + \bar{ABC}$$


$$\bar{B}(D+C) + \bar{B}\bar{C}\bar{D}$$

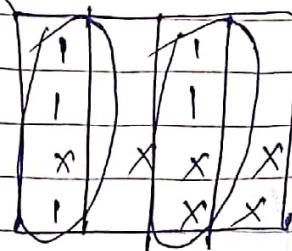

$\bar{a} \bar{D} + c D$

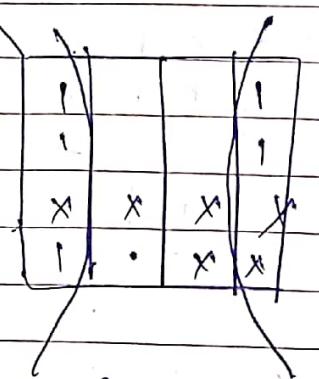

$\rightarrow \bar{P}$

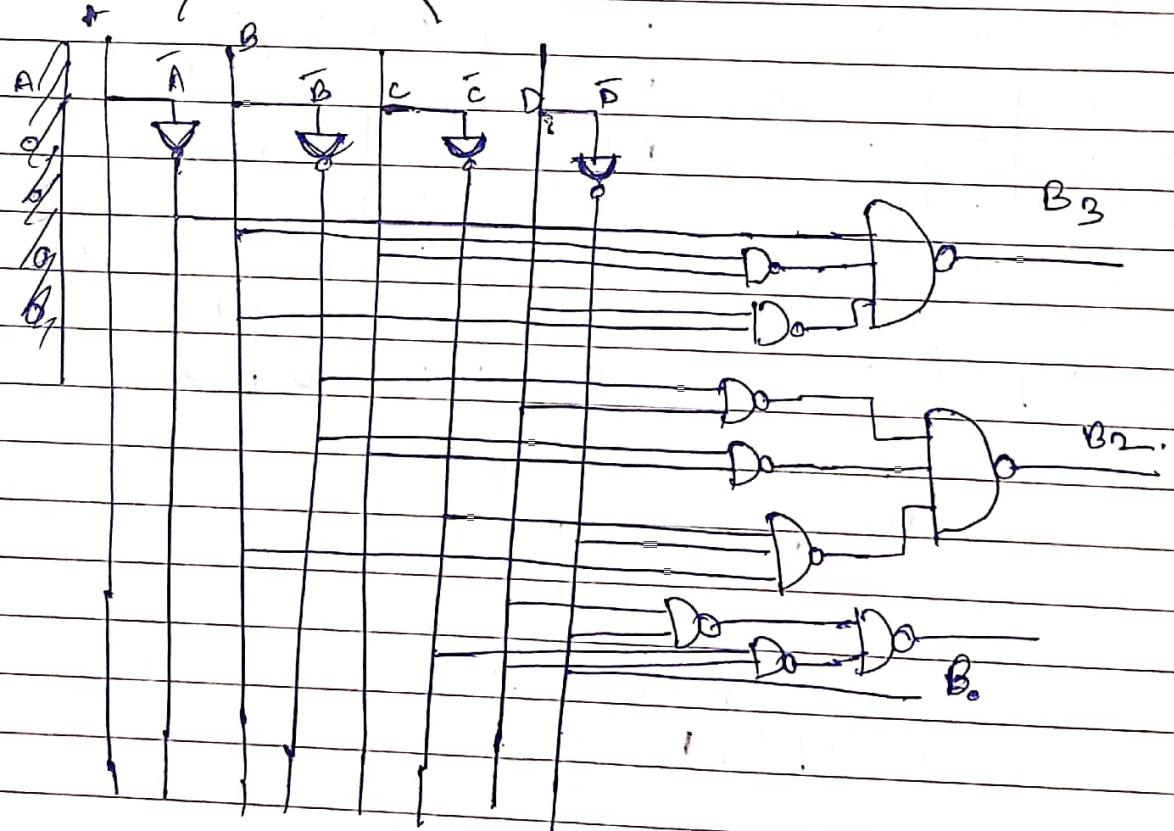

Binary to Gray Converter (4 variable).


	A	B	C	D	G	G ₁	G ₂	G ₃	G ₄	
0	0	0	0	0	0	0	0	0	0	.
1	0	0	0	1	0	0	0	1	1	.
2	0	0	1	0	0	0	1	1	3	.
3	0	0	1	1	0	0	1	0	2	.
4	0	1	0	0	0	1	1	0	6	.
5	0	1	0	1	0	1	1	1	7	.
6	0	1	1	0	0	1	0	1	5	.
7	0	1	1	1	0	1	0	0	4	.
8	1	0	0	0	1	1	0	0	12	.
9	1	0	0	1	1	1	0	1	13	.
10	1	0	1	0	1	1	1	1	15	.
11	1	0	1	1	1	1	1	0	14	.
12	1	1	0	0	1	0	1	0	10	.
13	1	1	0	1	1	0	1	1	11	.
14	1	1	1	0	1	0	0	0	9	.
15	1	1	1	1	1	0	0	0	8	.

	CD	$\bar{C}D$	$\bar{C}\bar{D}$	CD	$\bar{C}D$	$\bar{C}\bar{D}$
AB	00	01	11	10		
$\bar{A}B$	00	01	11	10		
$\bar{A}B$	01	11	10	00	01	11
AB	11	10	01	00	11	10
$A\bar{B}$	10	11	00	01	10	01

$$\overline{AB} + \overline{AD} + \overline{AC} \rightarrow A.$$


AB	CD	1	1	1	1
		1	1	1	1
		1	1	1	1
		1	1	1	1
		1	1	1	1

$$AB + \overline{AB}$$

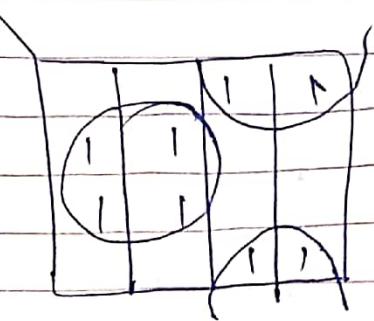


$$B\bar{C} + \bar{B}C$$


$$B \oplus C$$

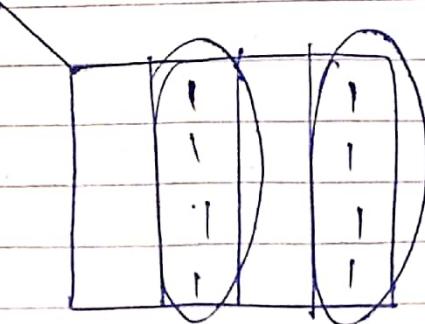


$$\bar{C}D + CD$$

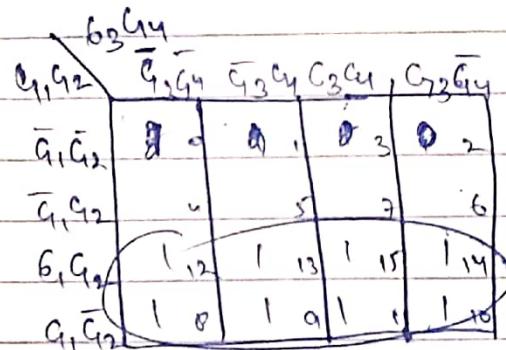


A

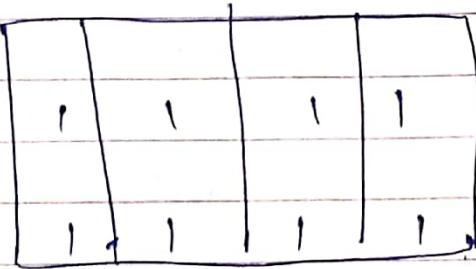


$$G\bar{1}G_2 + G_1\bar{G}_2.$$

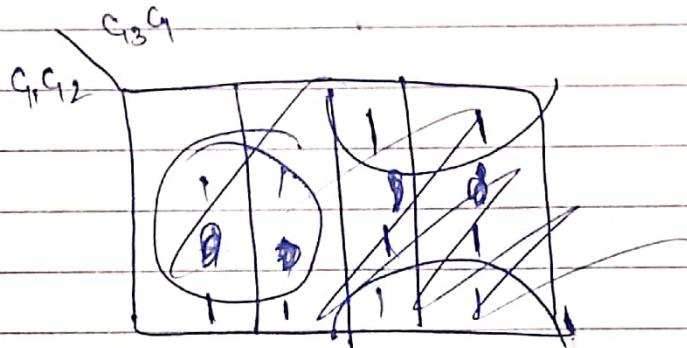


$$G_2\bar{G}_3 + G\bar{G}_3\bar{G}_2.$$

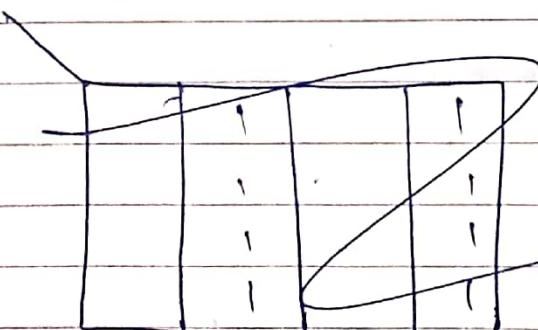


$$\bar{G}_3G_4 + G_3\bar{G}_4.$$

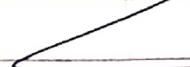

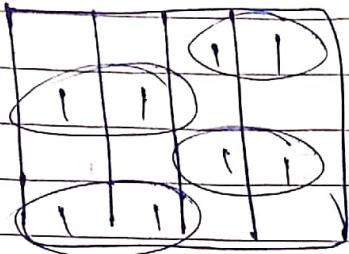
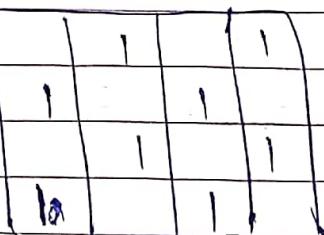
$$\bar{C}_1 \bar{C}_2 C_3 + \bar{C}_1 C_2 \bar{C}_3 + \\ C_1 C_2 C_3 + C_1 \bar{C}_2 \bar{C}_3. \\ C_1 \oplus C_2 \oplus C_3.$$



$$\bar{C}_1 \bar{C}_2 \bar{C}_3 C_4 + \bar{C}_1 \bar{C}_2 C_3 \bar{C}_4 + \\ \bar{C}_1 C_2 (C_3 \bar{C}_4 + C_3 C_4) + \\ C_1 C_2 (\bar{C}_3 C_4 + C_3 \bar{C}_4) + \\ C_1 \bar{C}_2 (\bar{C}_3 \bar{C}_4 + C_3 C_4).$$

$$\cancel{C_1} + (C_3 \oplus C_4)(C_1 \oplus C_2) + (C_3 \oplus C_4)(C_1 \oplus C_2)$$


$$\Rightarrow C_1 \oplus C_2 \oplus C_3 \oplus C_4$$


Programmable Logic devices :-

- ① Simple programmable logic devices (SPLD)
- ② Programmable logic array (PLA)
- ③ Programmable array logic (PAL)

Complex PLD.

Field Programmable Gate Array (FPGA)

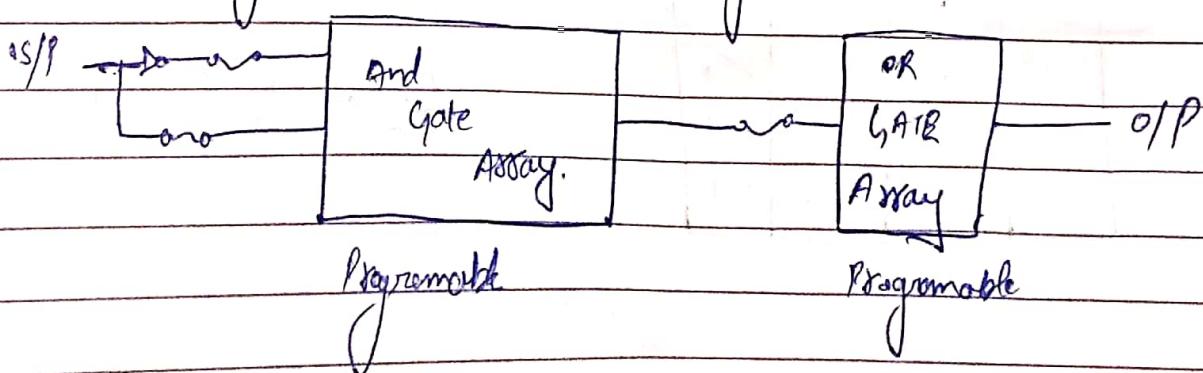


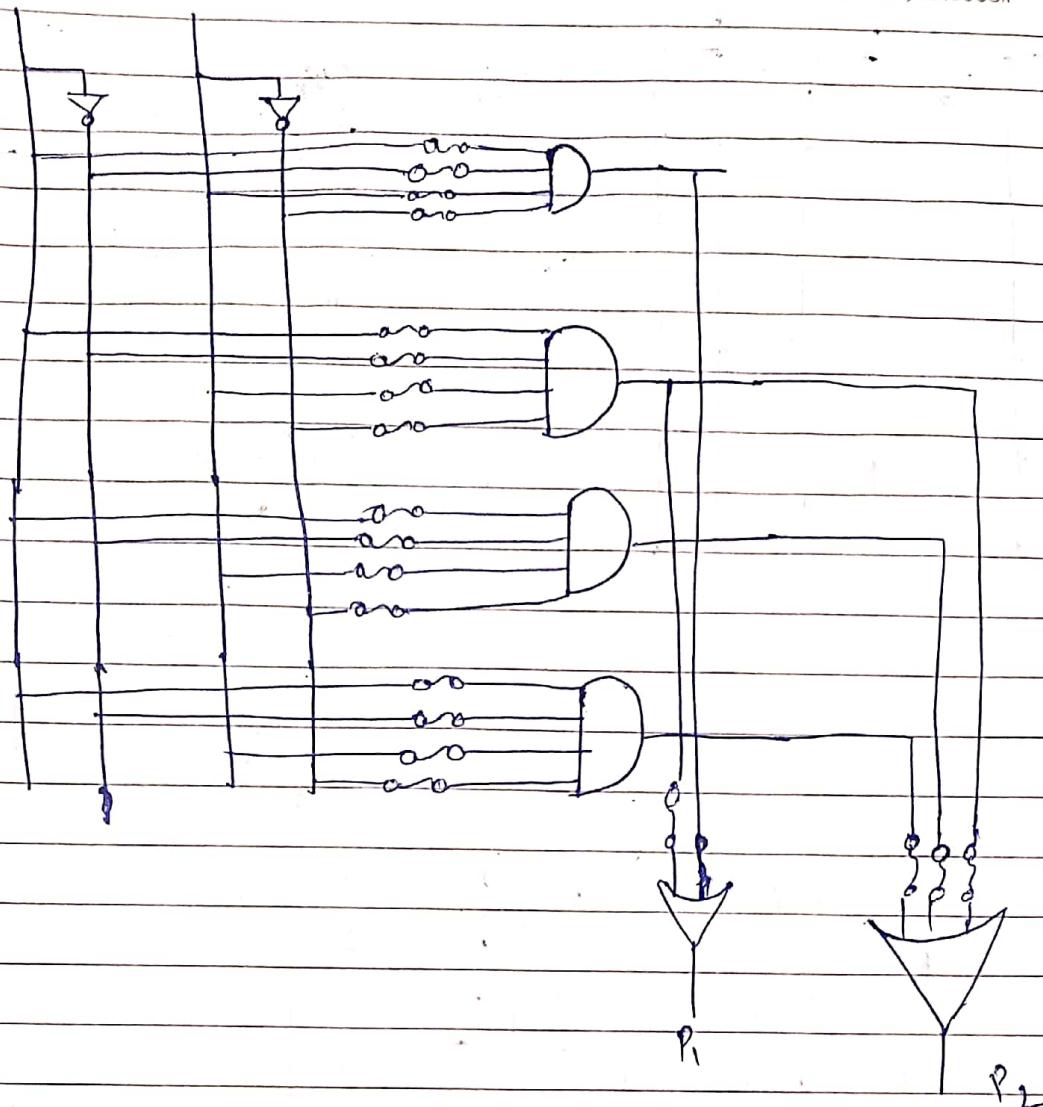


If both and and OR are programmable then it comes under category Programmable logic Array (PLA).

$$f_1(A, B, C) = \Sigma m(1, 5, 7)$$


$$f_2(A, B, C) = \Sigma m(5, 6, 7)$$

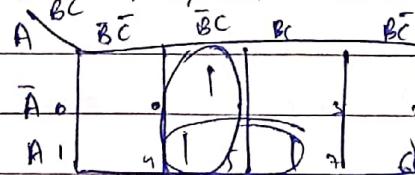

$$\bar{B}C + AC$$

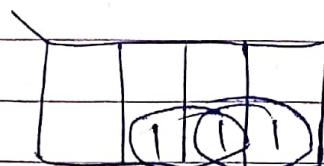

$$AC + AB$$


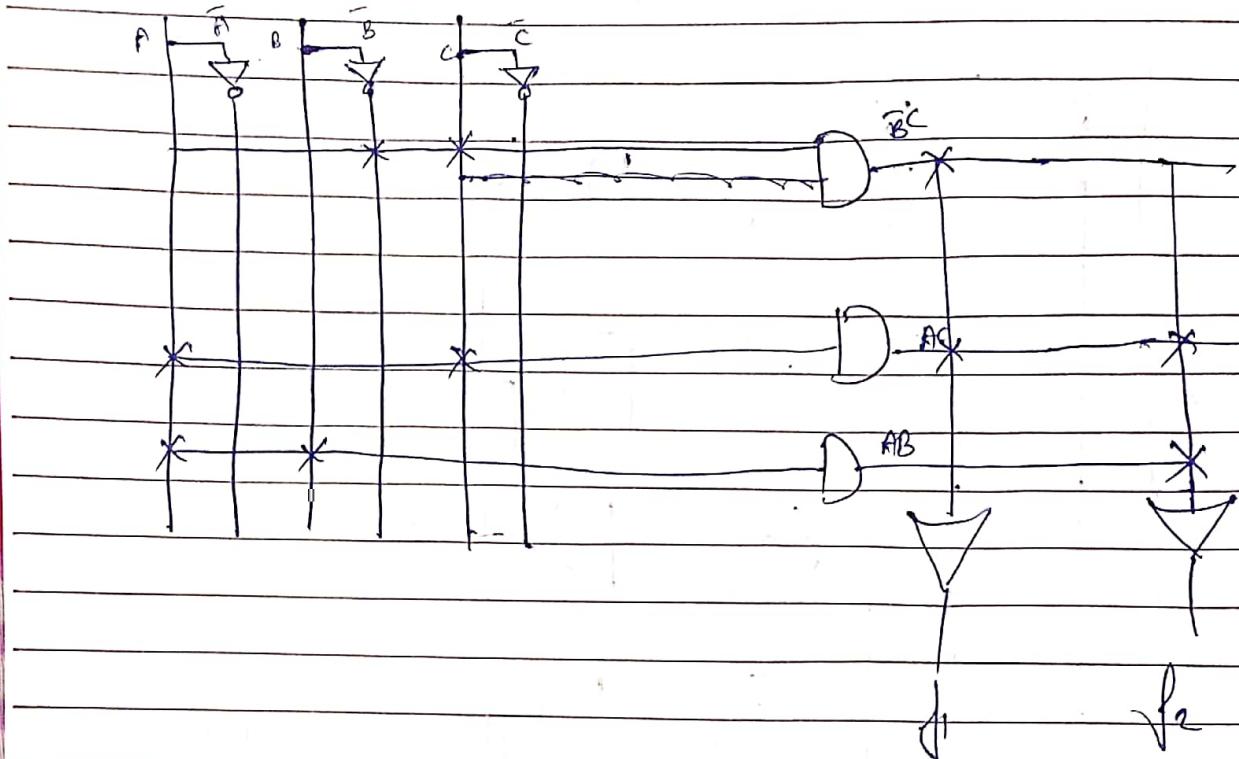


Product				OR
Term	A	B	C	f ₁
BC	-	0	1	1
AC	1	-	1	1
AB	1	1	-	1

Q) → A combinational logic circuit has 4 inputs and 2 outputs f_1 & f_2 . The output f_1 gives the high output when input combination is ≥ 1001 . (q) otherwise no output. The output f_2 gives high output when input combination is 1001 otherwise low.


$$f_1 = \Sigma m(9, 10, 11, 12, 13, 14, 15)$$
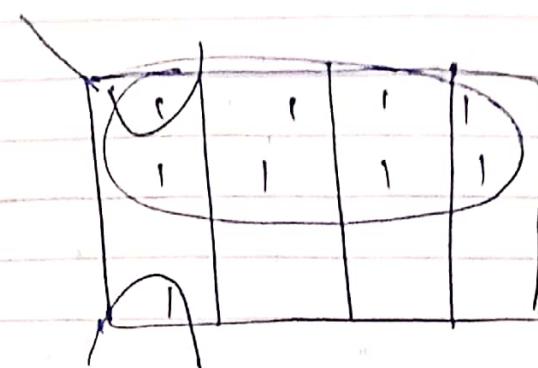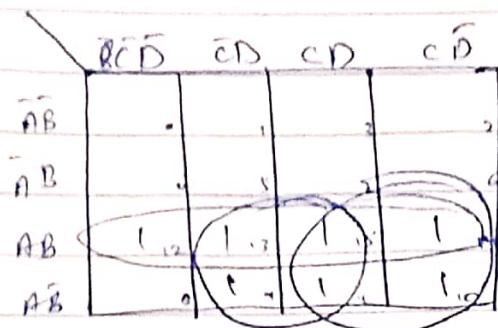
$$f_2 = \Sigma m(0, 8, 1, 7, 3, 4, 5, 6, 9, 8)$$



$$AB + AD + AC$$


$$\bar{A} + AB'C'D'$$

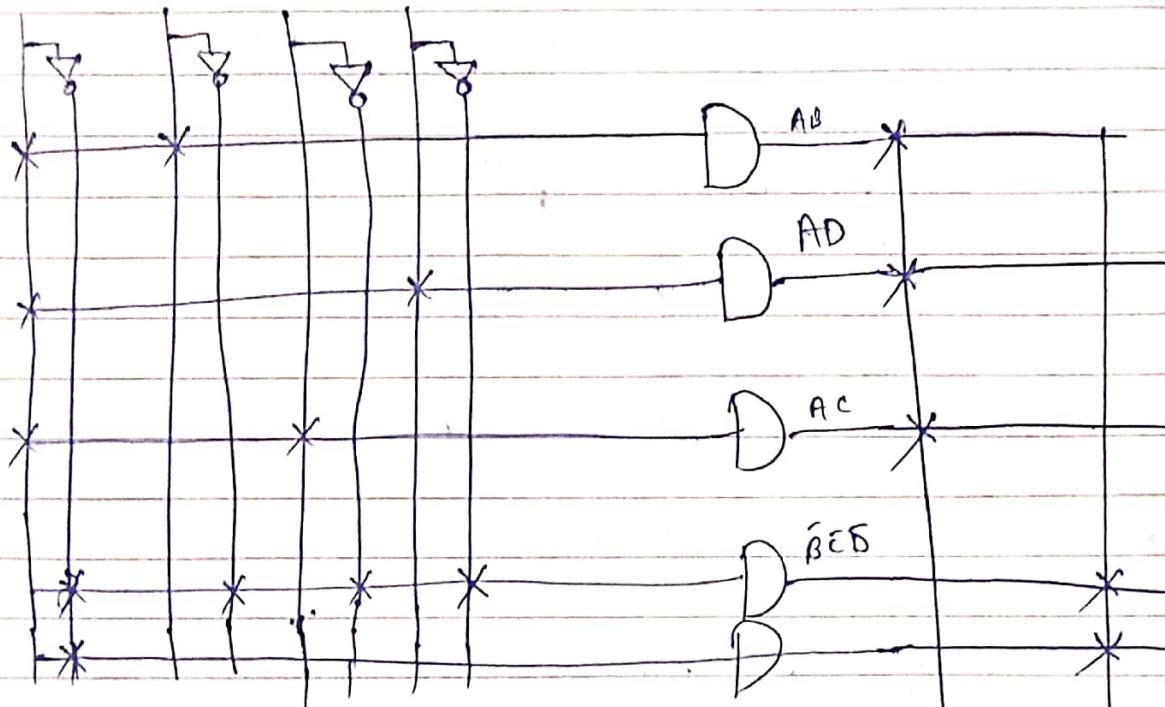

	J/P				O/P	
	A	B	C	D	f_1	f_2
AD	1	-	-	1	1	-
AC	1	-	1	-	1	-
AB	1	1	-	-	1	-
$\bar{B}\bar{C}\bar{D}$	-	0	0	0	-	1
\bar{A}	0	-	-	-	-	1

Path

programmable

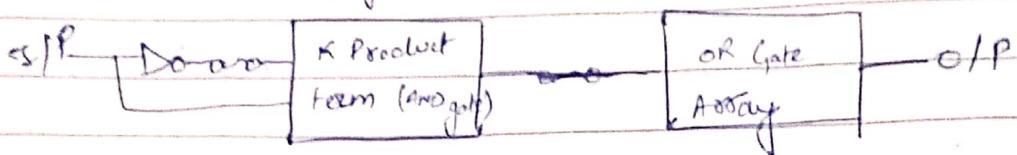

$$A(w, x, y, z) = \Sigma m(0, 2, 6, 7, 8, 9, 13, 15)$$

$$B(w, x, y, z) = \Sigma m(9, 7, 8, 9, 0, 2, 6, 12, 13, 14)$$

$$C(w, x, y, z) = \Sigma m(1, 3, 4, 6, 10, 12, 13)$$

$$D(w, x, y, z) = \Sigma m(1, 3, 4, 6, 9, 13, 14)$$

$wx\bar{y}\bar{z}$	$\bar{w}\bar{x}\bar{y}\bar{z}$	$\bar{w}y\bar{x}\bar{z}$	$w\bar{y}\bar{x}\bar{z}$	$w\bar{y}x\bar{z}$
$w\bar{x}y\bar{z}$	1	1	1	1
$w\bar{x}y\bar{z}$	1	1	1	1
$w\bar{x}y\bar{z}$	1	1	1	1


$$A = w\bar{y} + \bar{w}\bar{x}\bar{z} + \bar{w}xy$$

1	1	1
1	1	1
1	1	1


$$B = \cancel{w\bar{y}} + \bar{w}\bar{x}\bar{z} + \bar{w}xy + xy\bar{z}$$

1	1	1	1
1	1	1	1
1	1	1	1
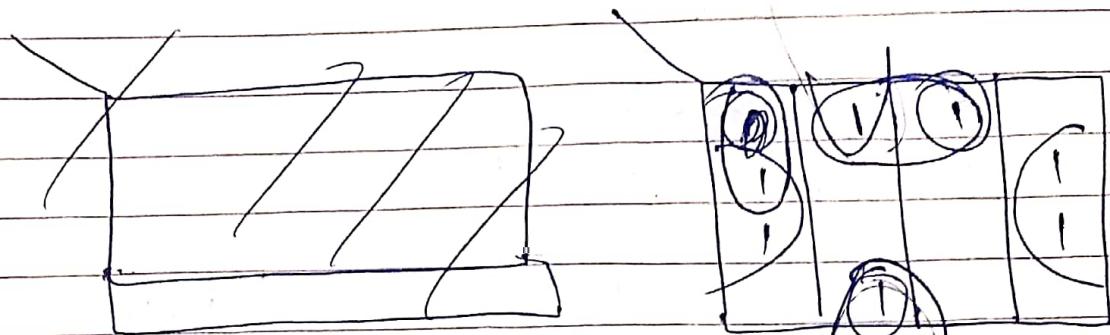
$$C = \bar{w}\bar{x}y + \bar{w}\bar{x}z + \bar{w}x\bar{z} + \bar{w}\bar{x}yz$$


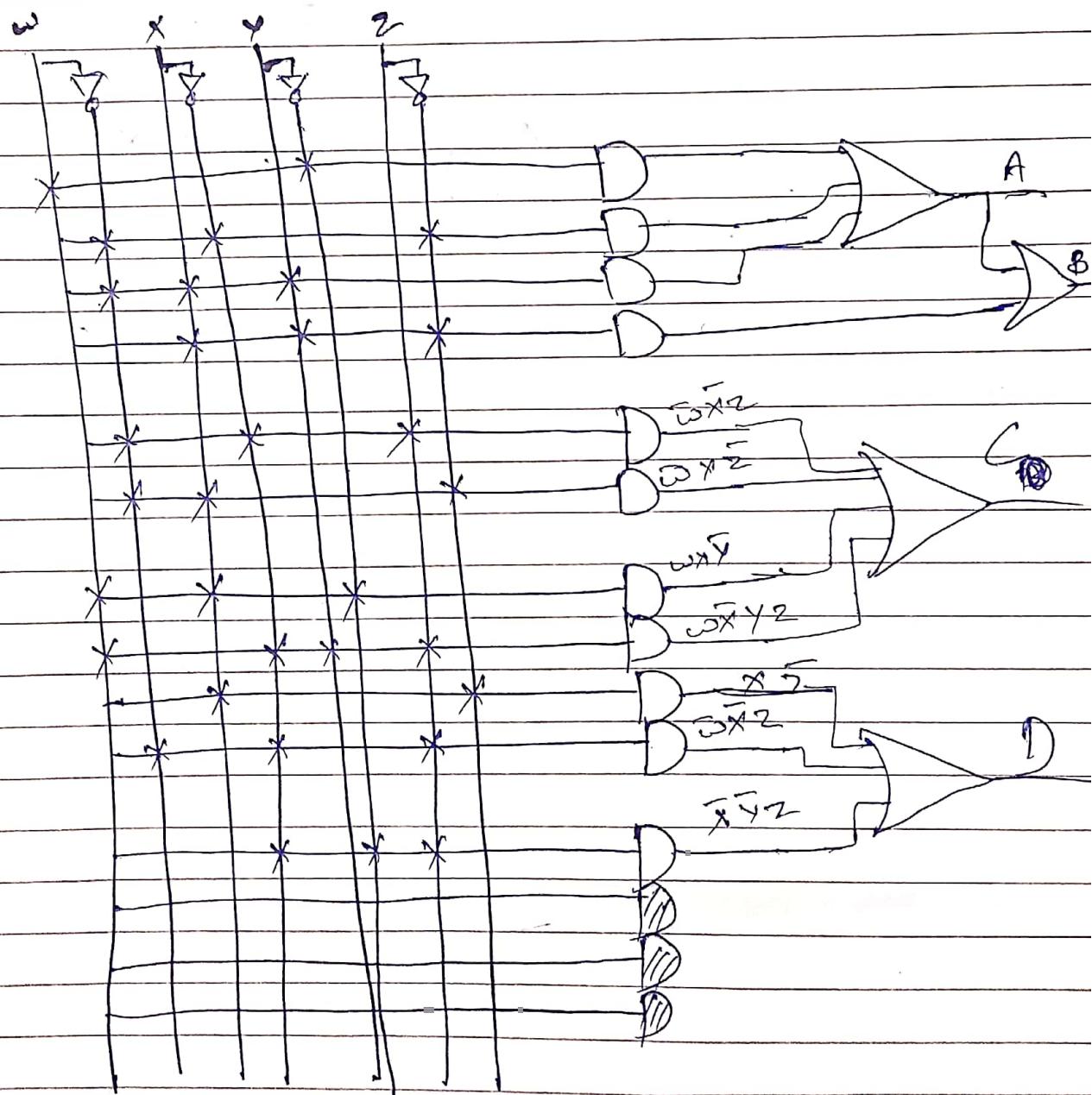
$$D = \bar{x}\bar{z} + \bar{w}\bar{x}\bar{z} + \bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}\bar{y}\bar{z}$$



ROM - (Read only memory) → And fixed but or
programmable.

$$A = \Sigma m(0, x, y)$$

$$B = \text{Sym}(1, 2, 3)$$

